

CSE 369 QUIZ 3

Name: Perry Perfect

Student ID
Number: 1234567

Please do not turn the page until 11:40.

Instructions

- This quiz contains 4 pages, including this cover page.
- Show scratch work for partial credit, but put your final answers in the boxes and blanks provided.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 60 (+10) minutes to complete this quiz.


Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.


Question	Points	Score
(1) Decoders	12	12
(2) Routing Elements	11	11
(3) Cryptography	9	9
Total:	32	32

 Question 1: Decoders [12 pts]

We are building a 7-seg decoder circuit for Simon, a color-based memory game with 4 buttons. The signals T(op), B(ottom), L(eft), and R(right) are high (1) only if a button in the corresponding column or row is being pushed. The 2-bit bus K represents which color is recognized (green = 00, red = 01, blue = 10, yellow = 11). The Valid signal (V) is high when at least one *button* is being pressed.




 - (A) Complete the truth table. We give priority to T and L. [4 pt]
- (B) In the space below, solve for the minimal logical expression for K_0 . [4 pt]



T	B	L	R	V	K ₁	K ₀
0	0	0	0	0	X	X
0	0	0	1	0	X	X
0	0	1	0	0	X	X
0	0	1	1	0	X	X
0	1	0	0	0	X	X
0	1	0	1	1	1	1
0	1	1	0	1	1	0
0	1	1	1	1	1	0
1	0	0	0	0	X	X
1	0	0	1	1	0	1
1	0	1	0	1	0	0
1	0	1	1	1	0	0
1	1	0	0	0	X	X
1	1	0	1	1	0	1
1	1	1	0	1	0	0
1	1	1	1	1	0	0


- (C) For the 7-seg signal numbering and outputs shown above (lit/red = 1), draw the minimal logic for S_2 in terms of V, K_1 , and K_0 . All signals should be off when $V = 0$. [4 pt]

 

Question 2: Routing Elements [11 pts]

We are creating a sequential circuit with 1-bit inputs E (enable), A (action), and D (direction) and n -bit output Q . When not enabled, Q stays constant, otherwise, the circuit will either count ($A=0$) or shift ($A=1$) each cycle. $D=0$ indicates to *decrement* when counting or *right-shift* when shifting and $D=1$ indicates the opposites. The circuit always shifts in a θ bit.

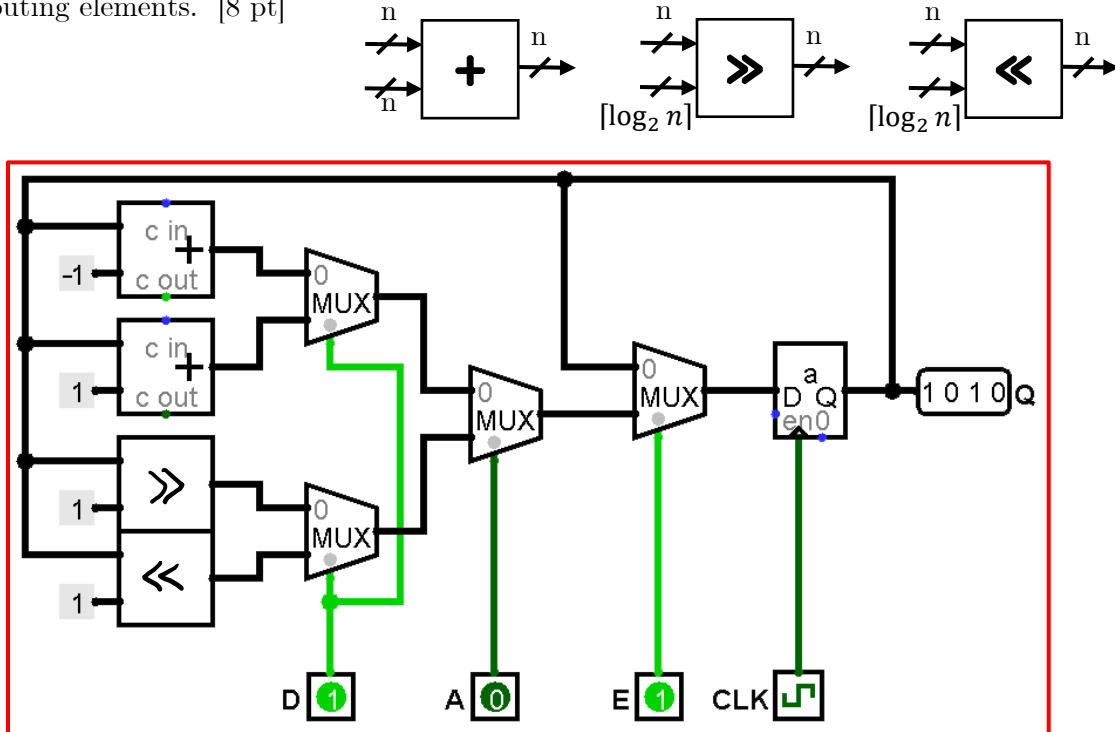- (A) Draw out the circuit below. You can freely use registers, constants, 2:1 MUXes, and the following logic blocks. Make sure you label the corresponding selector bits for ports of routing elements. [8 pt]



- (B) Now assume that we instantiate our circuit with $n = 3$. In the Verilog testbench below, fill in the blanks to indicate how the output of our sequential circuit updates. [3 pt]

```

initial begin
    D <= 1; A <= 0; E <= 1; // Q: 000
    @(posedge clk);
    A <= 1; // Q: 001 ( + 1 )
    @(posedge clk);
    E <= 0; // Q: 010 ( <<1 )
    @(posedge clk);
    D <= 0; A <= 0; E <= 1; // Q: 010 (  $\emptyset$  )
    @(posedge clk);
    A <= 1; // Q: 001 ( - 1 )
    @(posedge clk);
    A <= 0; // Q: 000 ( >>1 )
    @(posedge clk);
    $stop(); // Q: 111 ( - 1 )
end

```

Question 3: Cryptography [9 pts]


In cryptography, we wish to encode a message to apparent nonsense in a *reversible* manner so that the intended recipient can decode it and recover the original message. We can build a simple encoder using logic gates and a special “key”!

Example: With the message $0b1110$, and key $0b1010$, we get the encrypted message $0b0100$, from which we can recover the original message using the same key.

(A) (Circle one) Which type of gate will allow us to reversibly encrypt and decrypt? [1 pt]

- AND NAND NOR OR XNOR **XOR**

 (B) Below, implement a 4-bit encryption circuit that computes the encrypted message e from the original message m and key k . You may only use a *single type of 2-input logic gate*. [3 pt]



(C) Assume $t_{\text{NOT}} = 10$ ns, $t_{\text{AND}} = t_{\text{OR}} = 25$ ns, and $t_{\text{XOR}} = 40$ ns. Now we want to implement a decryption circuit that reverses the encryption. How much slower, if at all, would this decryption circuit be than the encryption circuit from Part B? [2 pt]

The decryption circuit is identical to the encryption circuit! 0 ns

(D) Outline (in writing) a possible solution to handling messages of any length (*e.g.*, ones that are much longer than the key), assuming that we only have one instance of the encryption circuit (*i.e.*, we can't spawn extra circuitry on the fly). [3 pt]

One possibility would be to use the encryption circuit along with shift registers, encrypting n -bits at a time. You would need to shift n bits of the message, the key, and the result every clock cycle. The result would need to either be sent serially or written into a large enough buffer.