

Design of Digital Circuits and Systems

ASM with Datapath I

Instructor: Justin Hsia

Teaching Assistants:

Colton Harris

Deepti Anoop

Gayathri Vadhyan

Jared Yoder


Lancelot Wathieu

Matthew Hung

Relevant Course Information




- ❖ Homework 2 late deadline tonight (4/11)
- ❖ Homework 3 due next Friday (4/19)
 - FIFO buffers & ASM charts
- ❖ Lab 2 reports due Friday (4/12), demos 4/15-19
 - Same lab demo slots for whole quarter
- ❖ Lab 3 due 4/26
 - Lab 3 + 4 are really ~1.5 weeks long, so don't wait!
- ❖ Quiz 2 next Thursday (4/18)
 - Memory (ROM, RAM, reg files)

Review: ASM Chart

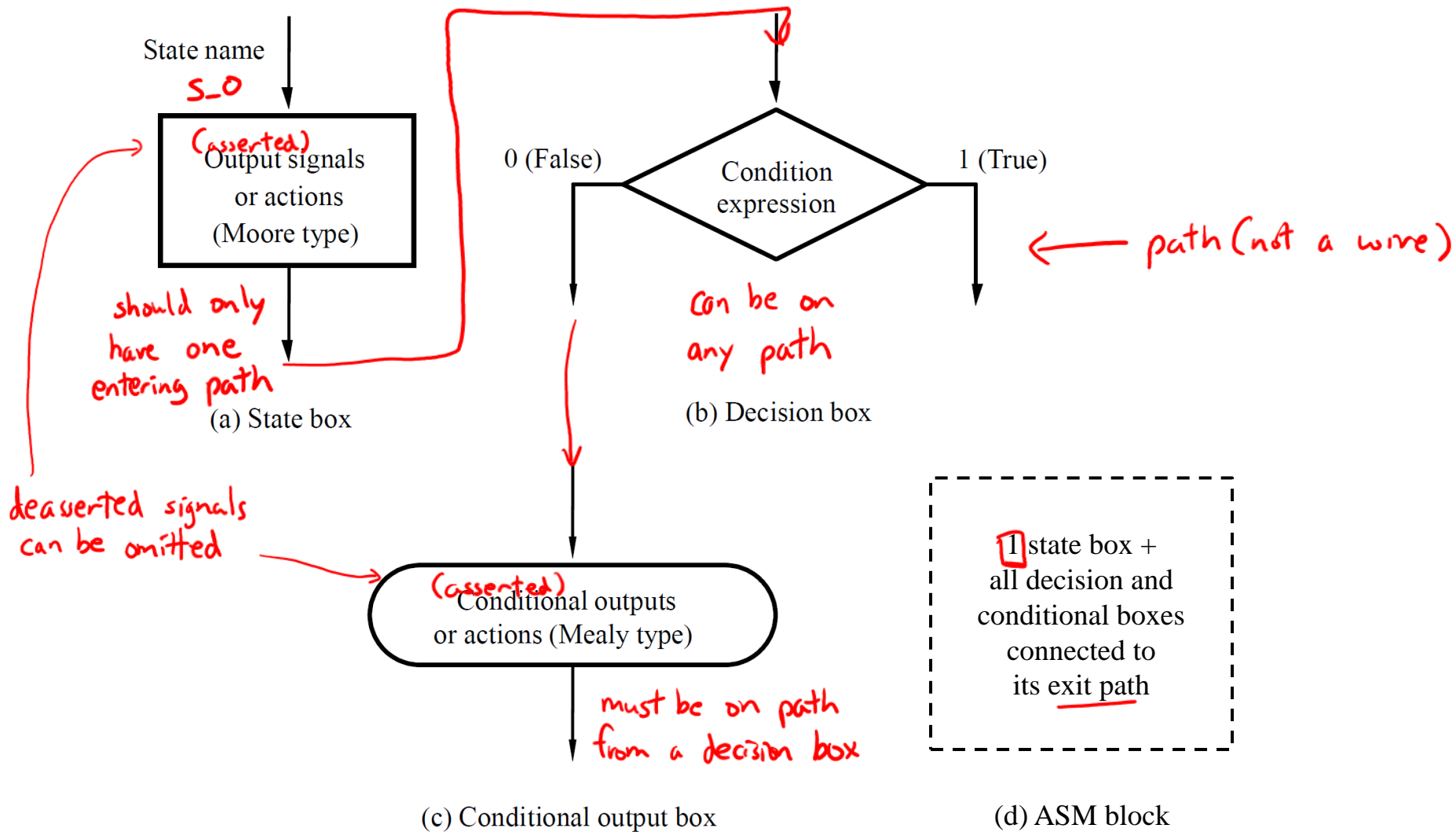


Review Question: 3-way Switch

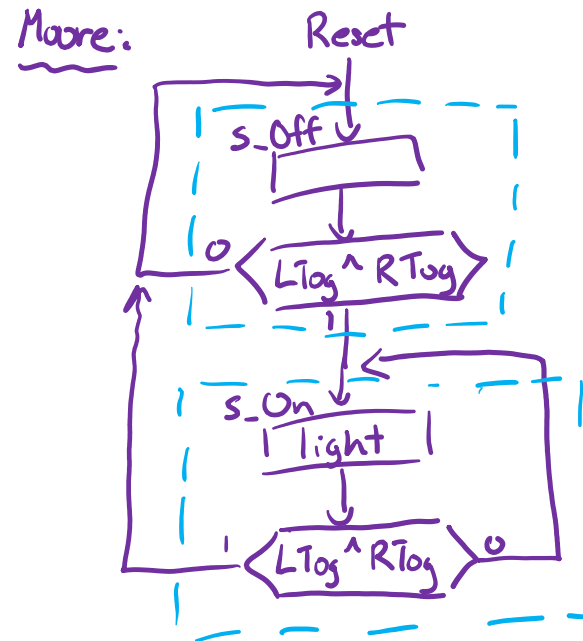  - ❖ Create an ASM chart for a 3-way switch system using *Mealy*-type output
 - LTog and RTog pulse 1 when switch is flipped/toggled, output called light



ASMD Charts

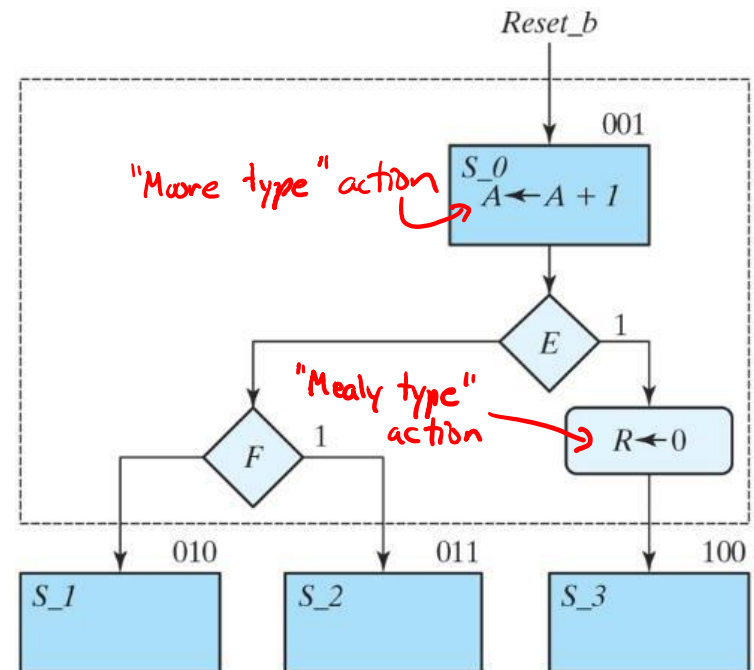- ❖ An **A**lgorithmic **S**tate **M**achine with a **D**atapath chart is created by adding RTL operations to an ASM chart
- ★ Timing of operations can be confusing – *NOT* a flowchart
- ❖ School of Thought #1:
 - RTL operations are triggered by control signals, so they can appear anywhere an output signal can:




ASMD Charts

- ❖ An **Algorithmic State Machine** with a **Datapath** chart is created by adding RTL operations to an ASM chart
 - Timing of operations can be confusing – *NOT* a flowchart


- ❖ School of Thought #2:
 - It's clearer to separate control signals (Control) from RTL operations (Datapath)

 - ❖ There isn't a set standard
 - You may see both or variants
 - ***We use School of Thought #2***




ASMD Hardware

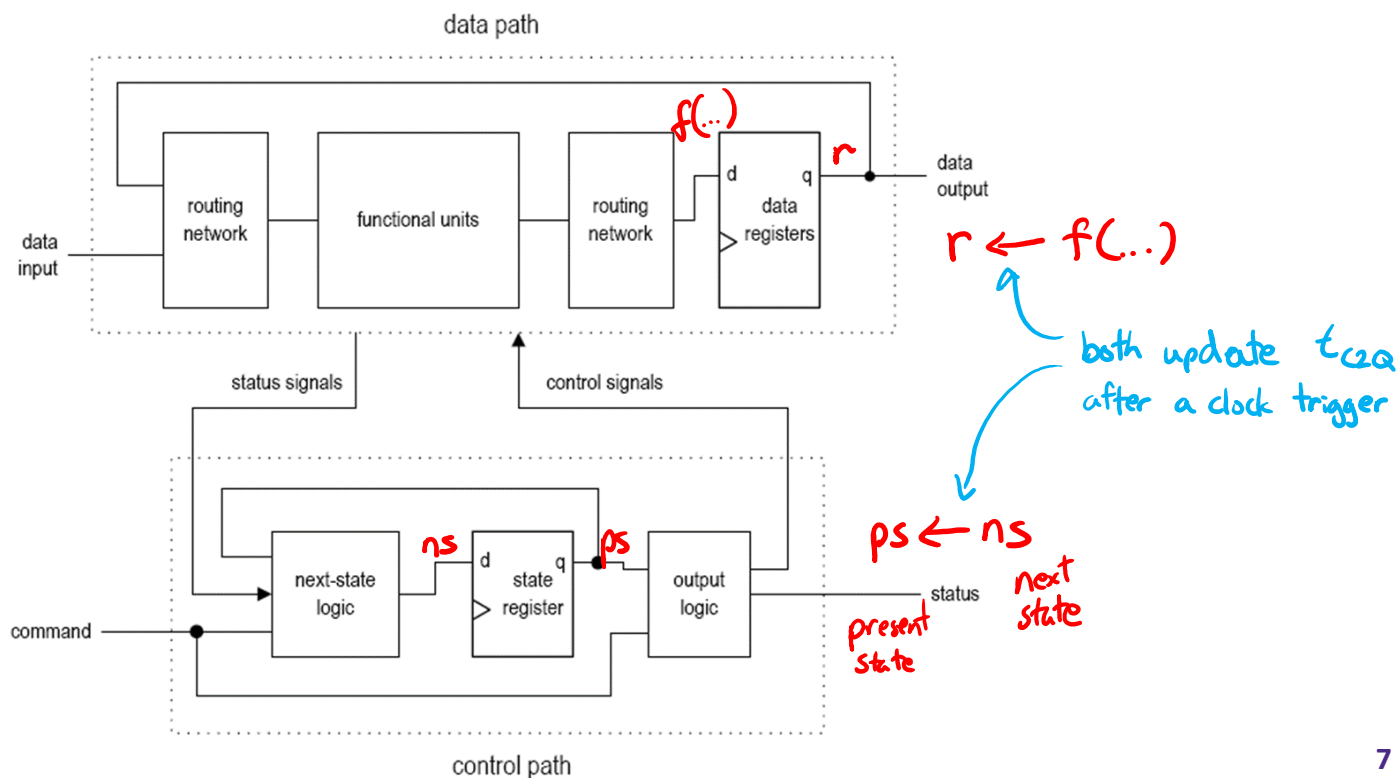- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!





ASMD Hardware

 - ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!
- ❖ The behavior of both state and data registers depend on the current control state
 - Can conceptually think of as a MUX to the registers' inputs that uses the current state as its selector bits





Hardware Example #1

 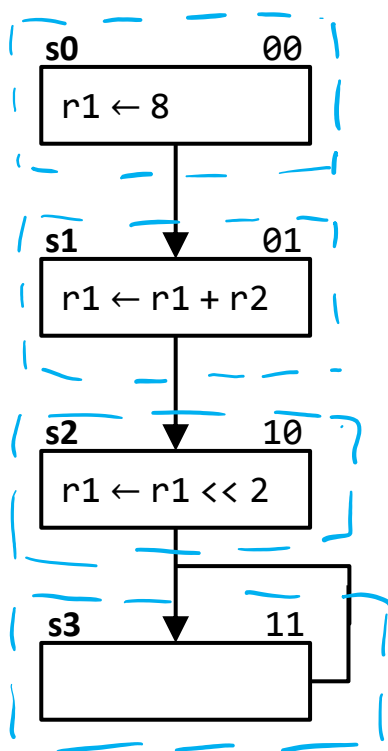- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!





Hardware Example #2

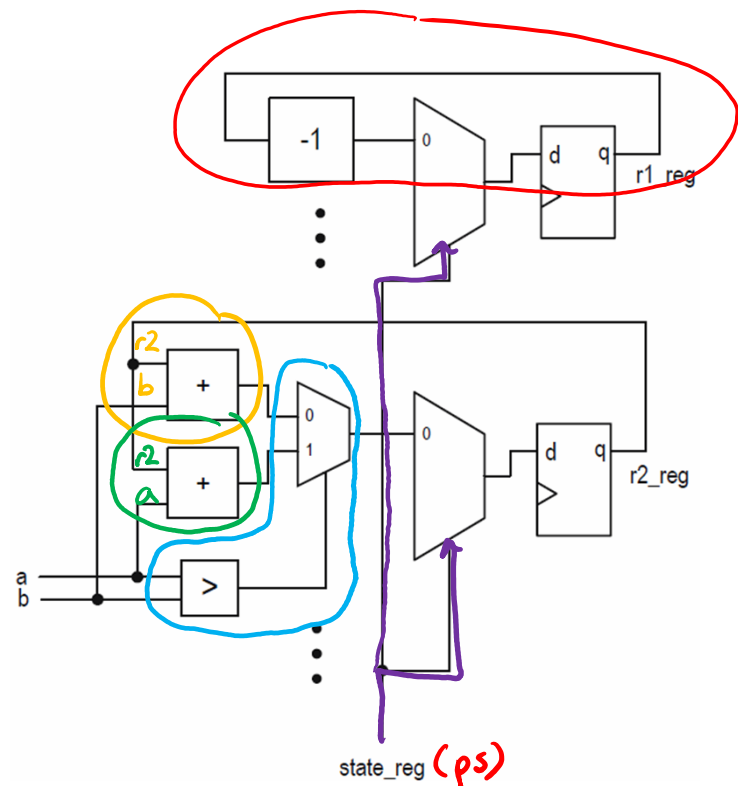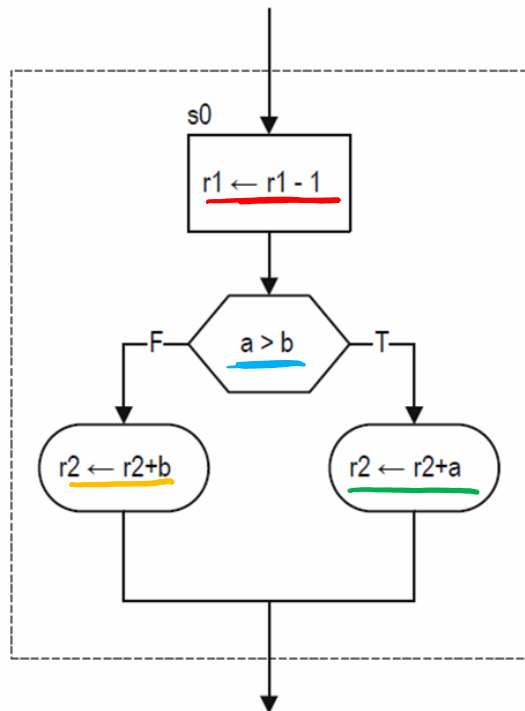- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!





ASMD Timing

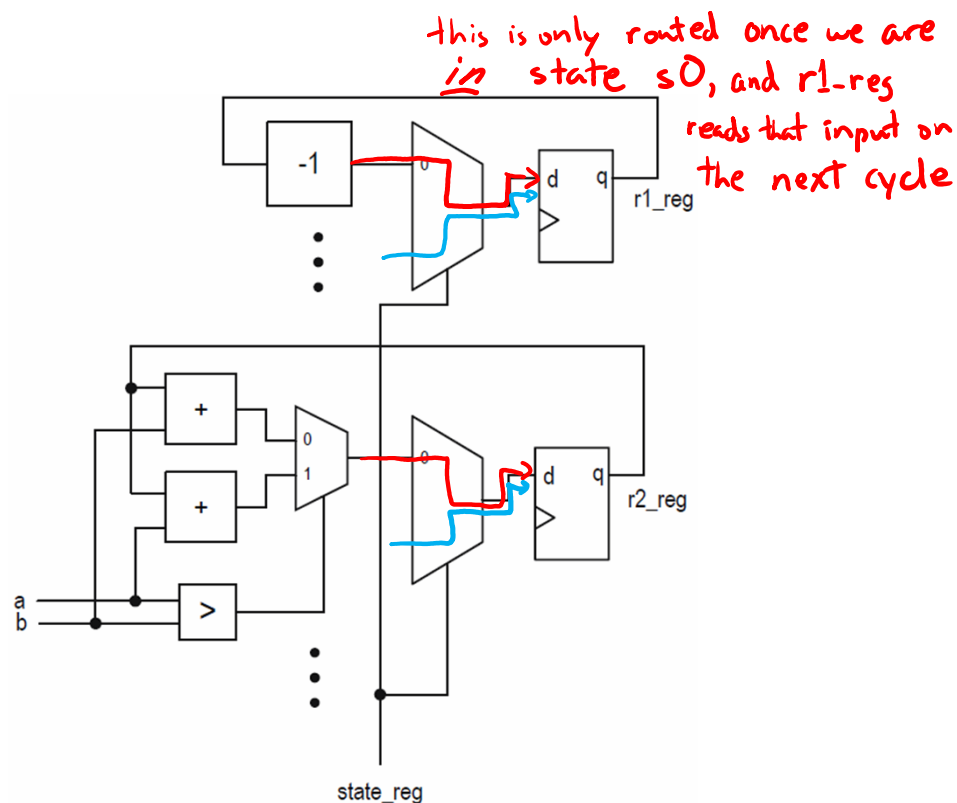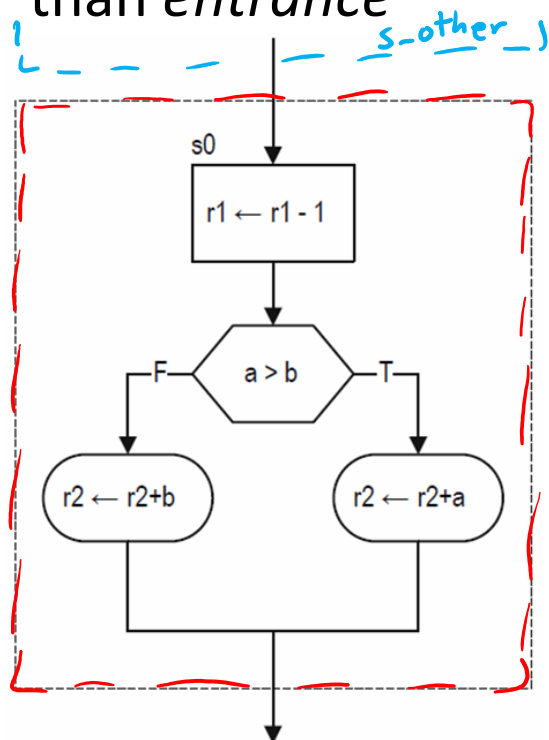- ❖ Everything (registers!) within an ASM block occurs simultaneously at the next clock trigger
 - Differs from a flowchart – changes occur at state exit rather than entrance



ASMD Timing

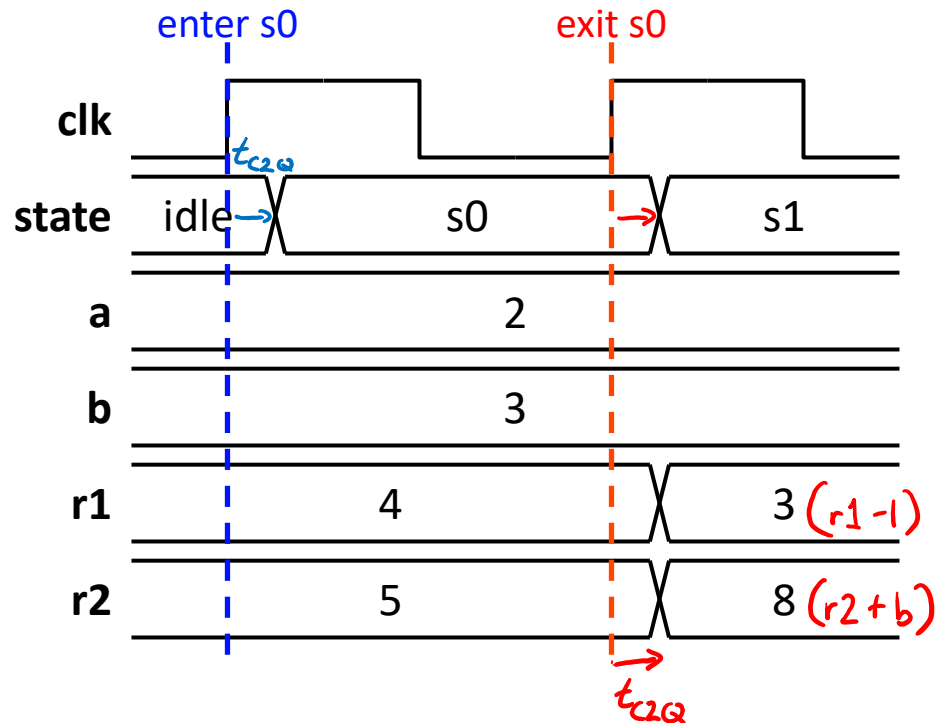
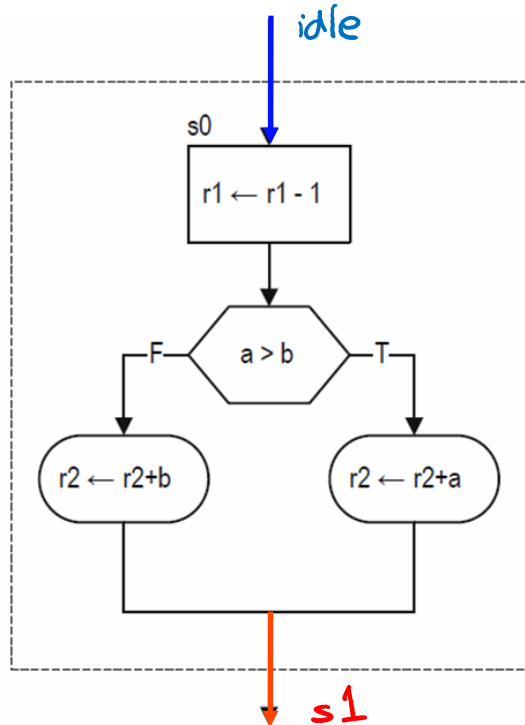
- ❖ Everything (registers!) within an ASM block occurs simultaneously at the next clock trigger
 - Differs from a flowchart – changes occur at state exit rather than entrance



ASMD Timing Question


- ❖ What value will be stored in r when we transition from state $s1$ to the next state? **-1**, 0, 1

  we exit when $r=0$, which means $0-1=-1$ is sitting on the input to r




ASMD Timing

 
- ❖ When a registered output (e.g., r) is used in a decision box, its effect may appear to be delayed by one clock
- Can define a next-state value (e.g., r_next) to use instead



(a) Use old value of r

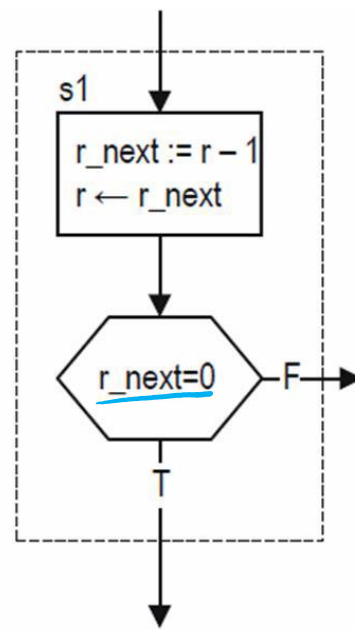

(b) Use new value of r

 


Short Tech Break

ASMD Design Procedure

- ❖ From problem description or algorithm pseudocode:
 - 1) Identify necessary datapath components and operations**
 - 2) Identify states and signals that cause state transitions** (external inputs and status signals), based on the necessary sequencing of operations
 - 3) Name the control signals** that are generated by the controller that cause the indicated operations in the datapath unit
 - 4) Form an ASM chart for your controller**, using states, decision boxes, and signals determined above
 - 5) Add the datapath RTL operations** associated with each control signal

Design Example #1

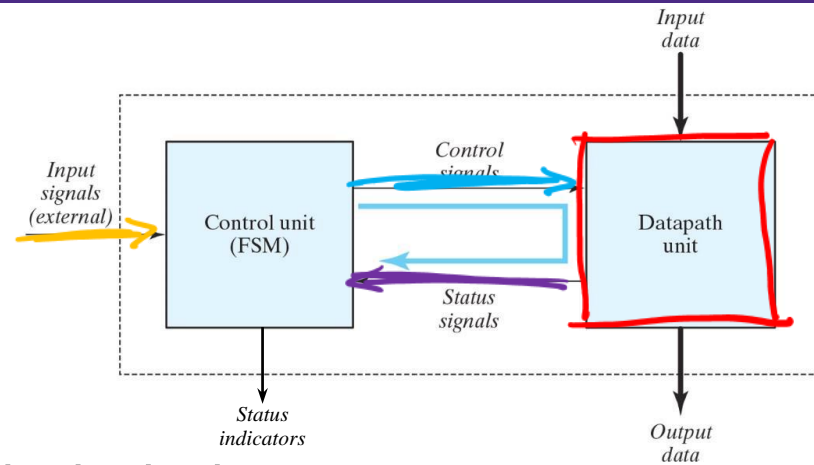


❖ System specification:

- datapath ■ Flip-flops E and F
- datapath ■ 4-bit binary up-counter A = $0bA_3A_2A_1A_0$
- inputs to control ■ Active-low reset signal $reset_b$ puts us in state S_idle , where we remain while signal $Start$ = 0
- control signals ■ $Start = 1$ initiates the system's operation by clearing A and F . At each subsequent clock pulse, the counter is incremented by 1 until the operations stop. ↑ clr_A-F
- status signals ■ Bits A_2 and A_3 determine the sequence of operations:
 - ↑ $incr_A$ • If $A_2 = 0$, set E to 0 and the count continues ← clr_E
 - control signals • If $A_2 = 1$, set E to 1; additionally, if $A_3 = 0$, the count continues, otherwise, wait one clock pulse to set F to 1 and stop counting (*i.e.*, back to S_idle) ↑ set_F

Design Example #1


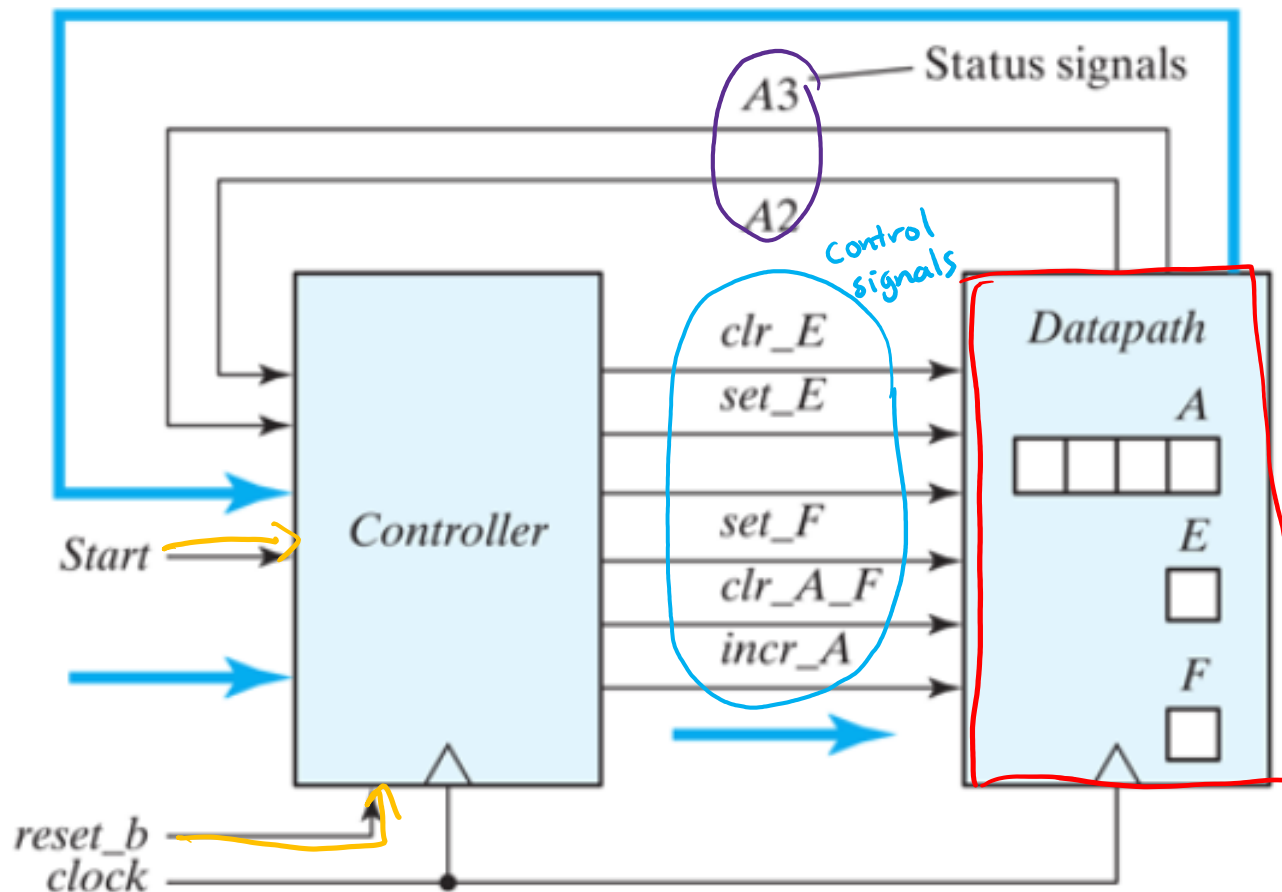
- ❖ The system can be represented by the following block diagram:



Design Example #1 (ASM → ASMD Chart)

- ❖ Synchronous or asynchronous reset?

  for synchronous reset, add decision box on reset-b out of every state box:



Design Example #1 (Timing)

❖ Sequence of operations:

| | | Counter | | | | Flip-Flops | | Conditions | State |
|-----------|---------|----------------|----------------|----------------|----------------|------------|---|--|---------|
| | | A ₃ | A ₂ | A ₁ | A ₀ | E | F | | |
| | | X | X | X | X | 1 | X | Start | S_idle |
| clr_A-F ↻ | clr_E ↻ | 0 | <u>0</u> | 0 | 0 | 1 | 0 | A ₂ = 0, A ₃ = 0 | S_count |
| | | 0 | 0 | 0 | 1 | 0 | 0 | | |
| | | 0 | 0 | 1 | 0 | 0 | 0 | | |
| | | 0 | 0 | 1 | 1 | 0 | 0 | | |
| set_E ↻ | | 0 | <u>1</u> | 0 | 0 | 0 | 0 | A ₂ = 1, A ₃ = 0 | |
| | | 0 | 1 | 0 | 1 | 1 | 0 | | |
| | | 0 | 1 | 1 | 0 | 1 | 0 | incr_A | |
| | | 0 | 1 | 1 | 1 | 1 | 0 | | |
| clr_E ↻ | | 1 | <u>0</u> | 0 | 0 | 1 | 0 | A ₂ = 0, A ₃ = 1 | |
| | | 1 | 0 | 0 | 1 | 0 | 0 | | |
| | | 1 | 0 | 1 | 0 | 0 | 0 | | |
| | | 1 | 0 | 1 | 1 | 0 | 0 | | |
| set_E ↻ | | 1 | <u>1</u> | 0 | 0 | 0 | 0 | A ₂ = 1, A ₃ = 1 | |
| | | 1 | 1 | 0 | 1 | 1 | 0 | | |
| | | 1 | 1 | 0 | 1 | 1 | 1 | | S_F |
| | | 1 | 1 | 0 | 1 | 1 | 1 | | S_idle |

Design Example #1 (Logic)

❖ Controller:

■ State Table:

$$S_idle = \bar{P}_1 \bar{P}_0$$

$$S_count = \bar{P}_1 P_0$$

$$S_F = P_1 P_0$$

state logic inputs ← → state logic outputs

| Present-State Symbol | Present State | | Inputs | | | Next State | | Outputs | | | | |
|----------------------|---------------|-------|--------|-------|-------|------------|-------|---------|-------|-------|---------|--------|
| | P_1 | P_0 | Start | A_2 | A_3 | N_1 | N_0 | set_E | clr_E | set_F | clr_A_F | incr_A |
| S_idle | 0 | 0 | 0 | X | X | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| S_idle | 0 | 0 | 1 | X | X | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| S_count | 0 | 1 | X | 0 | X | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| S_count | 0 | 1 | X | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| S_count | 0 | 1 | X | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| S_F | 1 | 1 | X | X | X | 0 | 0 | 0 | 0 | 1 | 0 | 0 |

■ Logic:

$$N_1 = S_count \cdot A_2 A_3 \qquad set_F = S_F$$

$$N_0 = S_count + S_idle \cdot Start \qquad clr_A_F = S_idle \cdot Start$$

$$set_E = S_count \cdot A_2 \qquad incr_A = S_count$$

$$clr_E = S_count \cdot \bar{A}_2$$

Short Tech Break

Design Example #1 (SV, Controller)

control signals (out)
 status signals (in)
 external inputs (in)

```

module controller (set_E, clr_E, set_F, clr_A_F,
                  incr_A, A2, A3, Start, clk,
                  reset_b);
// port definitions
input logic Start, clk, reset_b, A2, A3;
output logic set_E, clr_E, set_F, clr_A_F, incr_A;

```

// define state names and variables

```
enum logic [1:0] { S_idle, S_count, S_F = 2'b11 } ps, ns;
```

// controller logic w/synchronous reset

```
always_ff @(posedge clk)
```

```
  if (~reset_b)
```

```
    ps <= S_idle;
```

```
  else
```

```
    ps <= ns;
```

// asynchronous reset:

```
always_ff @(posedge clk, negedge reset_b)
```

```
  if (~reset_b)
```

```
    ps <= S_idle;
```

```
  else
```

```
    ps <= ns;
```


Design Example #1 (SV, Controller)

control signals (out)
status signals (in)
external inputs (in)

```
module controller (set_E, clr_E, set_F, clr_A_F,  
                 incr_A, A2, A3, Start, clk,  
                 reset_b);  
  
    // port definitions  
    input logic Start, clk, reset_b, A2, A3;  
    output logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // define state names and variables  
    enum logic [1:0] {S_idle, S_count, S_F = 2'b11} ps, ns;  
  
    // controller logic w/synchronous reset  
    always_ff @(posedge clk)  
        if (~reset_b)  
            ps <= S_idle;  
        else  
            ps <= ns;
```

Design Example #1 (SV, Controller)

```
// next state logic
```

```
always-comb  
case (ps)
```

```
    S_idle:    ns = Start ? S_count : S_idle;
```

```
    S_count:   ns = (A3 & A2) ? S_F : S_count;
```

```
    S_F:       ns = S_idle;
```

```
end case
```

```
// output assignments
```

```
assign set_E = (ps == S_count) & A2;
```

```
    .  
    .  
    .
```

```
endmodule // controller
```

Design Example #1 (SV, Controller)

```
// next state logic
always_comb
  case (ps)
    S_idle:    ns = Start ? S_count : S_idle;
    S_count:   ns = (A2 & A3) ? S_F : S_count;
    S_F:       ns = S_idle;
  endcase

// output assignments
assign set_E   = (ps == S_count) & A2;
assign clr_E   = (ps == S_count) & ~A2;
assign set_F   = (ps == S_F);
assign clr_A_F = (ps == S_idle) & Start;
assign incr_A  = (ps == S_count);

endmodule // controller
```

Design Example #1 (SV, Datapath)

control signals (in)
 status signals (out)
 external inputs (in)
 external outputs (out)

```
module datapath (A, E, F, clk, set_E, clr_E, set_F, clr_A_F,
                incr_A);
```

```
// port definitions
```

```
output logic [3:0] A;
```

```
output logic E, F;
```

```
input logic clk, set_E, clr_E, set_F, clr_A_F, incr_A;
```

```
// datapath logic
```

```
always_ff @(posedge clk) begin
```

```
    if (set_E) E <= 1;
```

```
    else if (clr_E) E <= 0;
```

```
    if (set_F) F <= 1;
```

```
    else if (clr_A_F) begin
```

```
        A <= 4'h0;
```

```
        F <= 0;
```

```
    end
```

```
    else if (incr_A) A <= A + 4'h1;
```

```
end
```

```
endmodule // datapath
```

} watch for potential conflicts!

Design Example #1 (SV, Datapath)

control signals (in)
status signals (out)
external inputs (in)
external outputs (out)

```
module datapath (A, E, F, clk, set_E, clr_E, set_F, clr_A_F,  
                incr_A);  
  
    // port definitions  
    output logic [3:0] A;  
    output logic E, F;  
    input logic clk, set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // datapath logic  
    always_ff @(posedge clk) begin  
        if (clr_E)      E <= 1'b0;  
        else if (set_E) E <= 1'b1;  
        if (clr_A_F)  
            begin  
                A <= 4'b0;  
                F <= 1'b0;  
            end  
        else if (set_F) F <= 1'b1;  
        else if (incr_A) A <= A + 4'h1;  
    end // always_ff  
  
endmodule // datapath
```

Design Example #1 (SV, Top-Level Design)

```
module top_level (A, E, F, clk, Start, reset_b);  
  
    // port definitions  
    output logic [3:0] A;  
    output logic E, F;  
    input  logic clk, Start, reset_b;  
  
    // internal signals (control signals and status signals that aren't outputs)  
    logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // instantiate controller and datapath  
    controller c_unit (.set_E, .clr_E, .set_F,  
                      .clr_A_F, .incr_A, .A2(A[2]),  
                      .A3(A[3]), .Start, .clk,  
                      .reset_b);  
  
    datapath d_unit (.*);  
  
endmodule // top_level
```