

# Design of Digital Circuits and Systems

## ASM with Datapath III

**Instructor:** Justin Hsia

**Teaching Assistants:**

Colton Harris

Deepti Anoop

Gayathri Vadhyan

Jared Yoder



Lancelot Wathieu

Matthew Hung

# Relevant Course Information

- ❖ Homework 3 due tomorrow
- ❖ Homework 4 released today and due 4/29
  - ASMDs and algorithm implementation debugging
- ❖ Quiz 2 (ROM, RAM, Reg files) @ 11:50 am
- ❖ Lab 3 reports due next Friday (4/26)
  - Ideally finish by early next week so you can start Lab 4
- ❖ Lab 4 released today and due 5/3
  - Implementing bit counting and binary search algorithms

# ASMD Chart Review Questions

  

❖ Circle all that apply:

■ Where can **control signals** be found?

State boxes <sup>outputs</sup> Decision boxes

■ Where can **status signals** be found?

State boxes <sup>inputs</sup> Decision boxes Conditional output boxes

■ Where can **external input signals** be found?

State boxes <sup>inputs</sup> Decision boxes Conditional output boxes

■ What is the *first* thing a path should encounter in an **ASM block**?

State boxes Decision boxes Conditional output boxes

■ What can be found outside of **ASM blocks**? *None!*

State boxes Decision boxes Conditional output boxes

■ What can **RTL operations** be attached to? <sup>for datapath</sup>


Control signals Status signals External output signals

Conditional output boxes
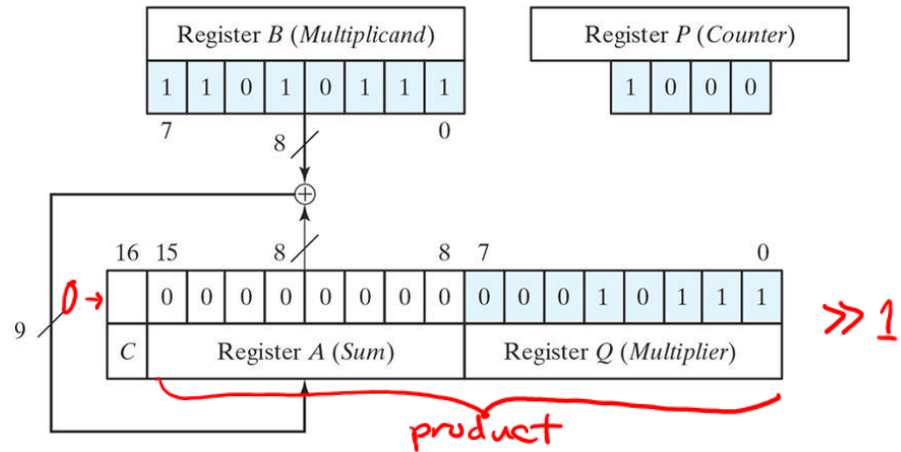
# Sequential Binary Multiplier Operation

❖ A few steps of:


$$\begin{array}{r} 11010111 \\ \times 00010111 \\ \hline \end{array}$$




Operation (completed)	C	A	Q	P
Initialize computation	0	00000000	00010111	1000
Add (Q[8]=1)	0	11010111	00010111	0111
Shift	0	01101011	10001011	0111
Add (Q[7]=1)	1	01000010	10001011	0110
Shift	0	10100001	01000101	0110
Add (Q[6]=1)	1	01111000	01000101	0101
Shift	0	10111100	00100010	0101

# Binary Multiplier (ASMD Chart)

States:

 

ASMD:

 

# ASMD Process Review

- 1) Identify datapath components, control signals, and status signals from description or pseudocode.
- 2) [*optional*] Create control-datapath circuit diagram.
- 3) [*optional*] Create state outline to plan out states and transitions between them.
- 4) Draw out ASM state boxes, decision boxes, and paths between them.
- 5) Augment state boxes with Moore-type outputs and add conditional output boxes with Mealy-type outputs.
- 6) Add ASM blocks to organize states.
- 7) Add RTL operations to control signals.
- 8) Double-check decision box edge cases and timing of operations (*i.e.*, debug).

# Short Tech Break

# Division Circuit

- ❖ Design a circuit that implements the long-division algorithm:

$$\begin{array}{r} 15 \\ 9 \overline{) 140} \\ \underline{9} \phantom{0} \\ 50 \\ \underline{45} \\ 5 \end{array}$$

(a) An example using decimal numbers

divisor → 1001

$$\begin{array}{r} 00001111 \quad \leftarrow \text{quotient} \\ \hline 10001100 \quad \leftarrow \text{dividend} \\ \underline{1001} \phantom{00} \\ 10001 \phantom{00} \\ \underline{1001} \phantom{00} \\ 10000 \phantom{00} \\ \underline{1001} \phantom{00} \\ 1110 \\ \underline{1001} \\ 101 \quad \leftarrow \text{remainder} \end{array}$$

(b) Using binary numbers

- ❖ Considerations:


- Main operations? *shift, subtract, compare*
- Stop condition? *n iterations if both divisor and dividend are n bits*



# Division Circuit

- ❖ Design a circuit that implements the long-division algorithm:
  - 1) Double the **dividend** width by appending 0's in front and align the **divisor** to the leftmost bit of the *extended dividend*.
  - 2) If the corresponding **dividend** bits are  $\geq$  the **divisor**, subtract the **divisor** from the **dividend** bits and make the corresponding **quotient** bit 1. Otherwise, keep the original **dividend** bits and make the **quotient** bit 0.
  - 3) Append one additional **dividend** bit to the previous result and shift the divisor to the right one position.
  - 4) Repeat steps 2 and 3 until all dividend bits are used.

# Division Circuit

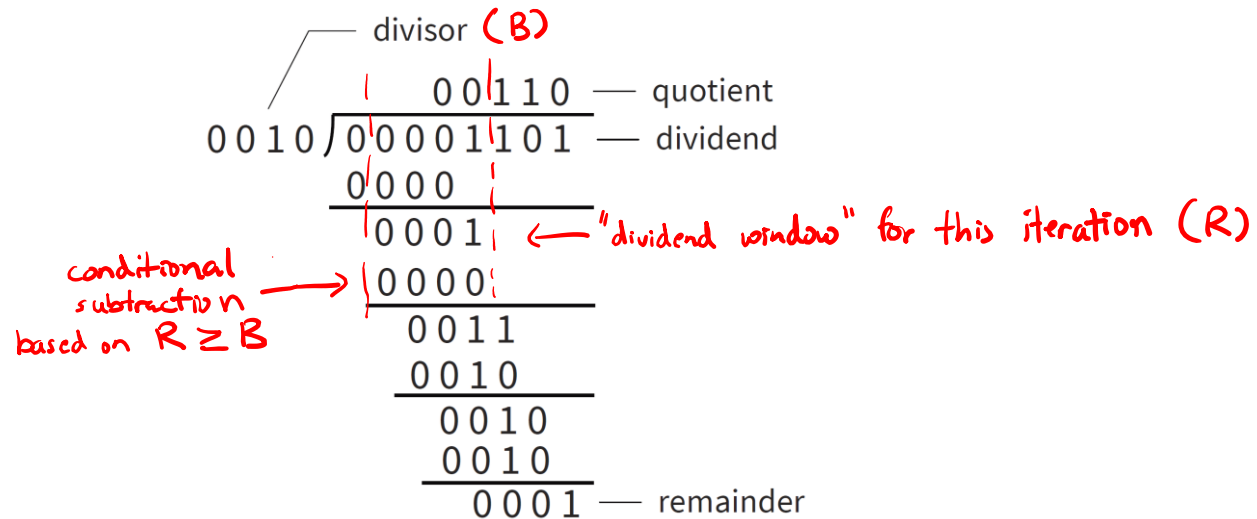

## ❖ Implementation Notes:

- If current **dividend window** is smaller than the **divisor**, skip subtraction
- Instead of shifting **divisor** to the right, we will shift the **dividend** (and the **quotient**) *to the left*
- We will re-use the lower half of the **dividend** register to store the **quotient**


# Division Circuit Operation

❖ A few steps of:

final Q → 0111 (7)  
 (2)0010 | 1111 (15)  

$$\begin{array}{r} 0010 \overline{) 1111} \\ \underline{-10} \phantom{00} \\ 110 \phantom{0} \\ \underline{-10} \phantom{00} \\ 100 \phantom{0} \\ \underline{-10} \\ 0001 \end{array}$$
  
 final R → 0001  
 registers

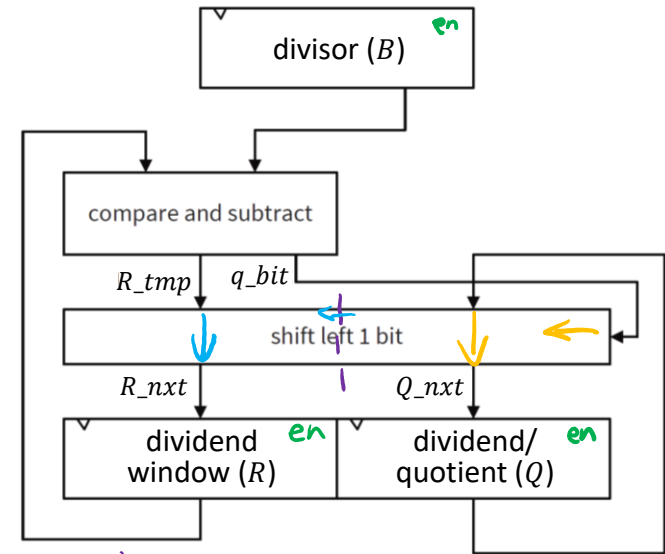$q\_bit = (R \geq B)$   
 $Q\_nxt = \{Q[a-2:0], q\_bit\}$   
 $R\_tmp = q\_bit ? R - B : R$   
 $R\_nxt = \{R\_tmp[a-2:0], Q[a-1]\}$



Op (done)	B	R	Q	q_bit	R_tmp	R_nxt	Q_nxt	P
Initialize	0010	0000 ↓ R_nxt	<u>1111</u> ↓ Q_nxt	<u>0</u>	<u>0000</u> (R)	<u>0001</u>	<u>1110</u>	100
Compute	0010	0001 ↓ R_nxt	1110 ↓ Q_nxt	0	0001 (R)	0011	1100	011
Compute	0010	0011 ↓ R_nxt	1100 ↓ Q_nxt	1	0001 (R-B)	0011	1001	010
Compute	0010	0011 ↓ R_nxt	1001 ↓ Q_nxt	1	0001 (R-B)	0011	0011	001
Compute	0010	0011 ↓ R_nxt	0011 ↓ Q_nxt	1	0001 (R-B)	0010	0111	000
Done	0010	0001 ↓ R_tmp	0111 ↓ Q_nxt	X	X	X	X	X

# Division Circuit Specification

## ❖ Datapath


- $2n$ -bit *register* with bits split into  $n$ -bit  $R$  and  $n$ -bit  $Q$
- Divisor stored in register  $B$ , dividend stored in  $Q$ ,  $R$  holds 0
- }
{
}
  - A “compare and subtract” module outputs  $\{R, 0\}$  if  $R < B$  and  $\{R - B, 1\}$  otherwise ( $\{R\_tmp, q\_bit\}$ )
  - A *shifter* left shifts  $q\_bit$  into  $\{R\_tmp, Q\}$  and outputs to the inputs of  $R$  and  $Q$
- A  $\lceil \log_2(n + 1) \rceil$ -bit *counter*  $P$

## ❖ Control


- Inputs *Start* and *Reset*, outputs *Ready* and *Done*
- Status signals:  $P\_zero$  (or all of  $P$ )
- Control signals:  $Load\_regs$ ,  $Enable\_RQ$ ,  $Finish\_RQ$ ,  $Decr\_P$

# Division Circuit (ASMD Chart)

States:

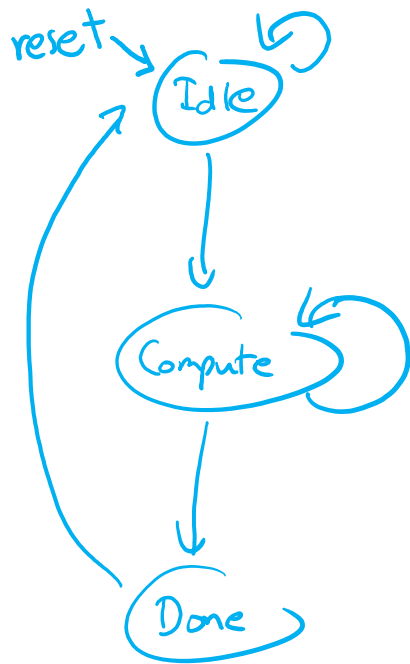

ASMD:

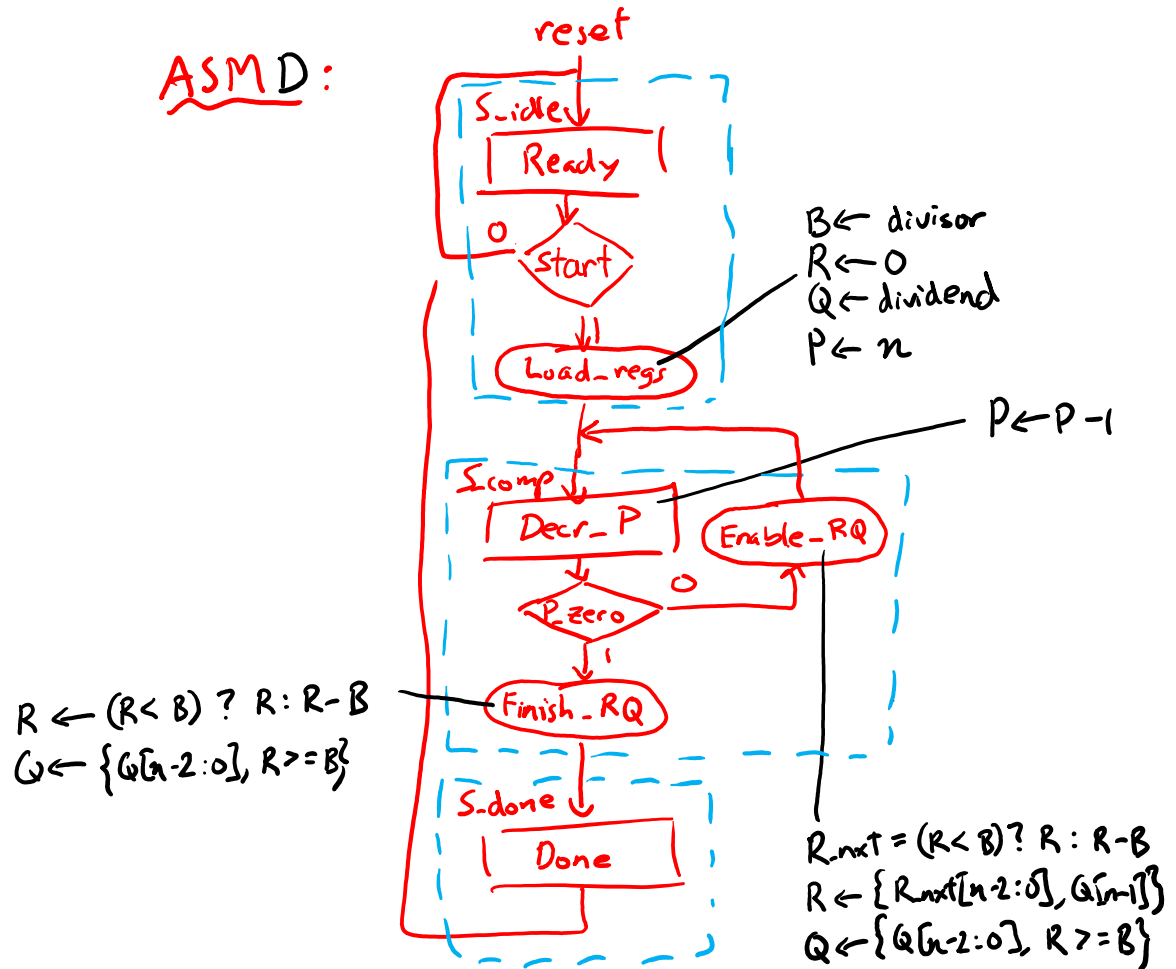

# Division Circuit Implementation

## ❖ Controller Logic

$$Load\_regs = S\_idle \cdot Start$$

$$Enable\_RQ = S\_comp \cdot \overline{P\_zero}$$

$$Finish\_RQ = S\_comp \cdot P\_zero$$

$$Decr\_P = S\_comp$$

$$Ready = S\_idle$$

$$Done = S\_done$$

# Division Circuit (SV, Datapath)

```
module datapath #(parameter WIDTH=4)
    (Q, P, divisor, dividend, clk,
     Load_regs, Enable_RQ, Enable_R, Decr_P);

    // port definitions
    output logic [2*WIDTH-1:0] product;
    output logic [WIDTH-1:0] Q, P; // note: unnecessary bits for P
    input logic [WIDTH-1:0] multiplicand, multiplier;
    input logic clk, Load_regs, Shift_regs, Add_regs, Decr_P;

    // internal logic
    logic [WIDTH-1:0] B, R, R_tmp, R_nxt;
    logic q_bit;

endmodule
```

# Division Circuit (SV, Datapath)

```
module datapath #(parameter WIDTH=4)
    (Q, P, divisor, dividend, clk,
     Load_regs, Enable_RQ, Enable_R, Decr_P);

    // port definitions & internal logic
    ...

    // assignments
    assign q_bit = (R >= B);
    assign R_tmp = (R < B) ? R : R-B;
    assign R_nxt = {R_tmp[WIDTH-2:0], Q[WIDTH-1]};
    assign Q_nxt = {Q[WIDTH-2:0], q_bit};

    // datapath logic
    always_ff @(posedge clk) begin
        if (Load_regs) begin
            R <= 0;      Q <= dividend;
            P <= WIDTH; B <= divisor;
        end
        if (Decr_P)      P <= P - 1;
        if (Comp_regs)  {R, Q} <= {R_nxt, Q_nxt};
        if (Done_regs)  {R, Q} <= {R_tmp, Q_nxt};
    end // always_ff

endmodule
```



# Lab 4 Preview: Bit Counter

- ❖ Design a circuit that counts the number of bits in a register  $A$  that have the value 1
- ❖ Algorithm:

```
B = 0; // counter
while A != 0 do
    if A[0] = 1 then
        B = B + 1
    endif
    A = A >> 1
endwhile
```