

Design of Digital Circuits and Systems

Algorithms to Hardware I

Instructor: Justin Hsia

Teaching Assistants:

Colton Harris

Deepti Anoop

Gayathri Vadhyan

Jared Yoder

Lancelot Wathieu

Matthew Hung

Relevant Course Information

- ❖ Lab 3 reports due Friday (4/26)
- ❖ Lab 4 due next Friday (5/3)
- ❖ hw4 due on Monday (4/29)
- ❖ Anonymous mid-quarter survey on Canvas (due 4/29)
- ❖ Quiz 3 (ASM, ASMD) next Thursday (5/2)

Arithmetic Mean

- ❖ Design a sequential circuit that computes the mean M of k n -bit numbers stored in registers
 - *e.g.*, accessing a RAM or register file with k addresses
 - To save on hardware, you can only use one n -bit adder and have a single read port RAM
- ❖ Algorithm Pseudocode:

Arithmetic Mean Specification

❖ Datapath

- A k -address *register file* (only using `r_addr` and `r_data`)
- Reg file address stored in $\lceil \log_2(k) \rceil$ *down-counter* A
- Sum stored in register S
- An n -bit *divider* circuit, as discussed last lecture

❖ Control


- Inputs *Start* and *Reset*, outputs *Ready* and *Done*
- Status signals:
- Control signals:

Arithmetic Mean (ASMD Chart, Initial)


- ❖ For now, ignore the details of the divider circuit

Arithmetic Mean (ASMD Chart)

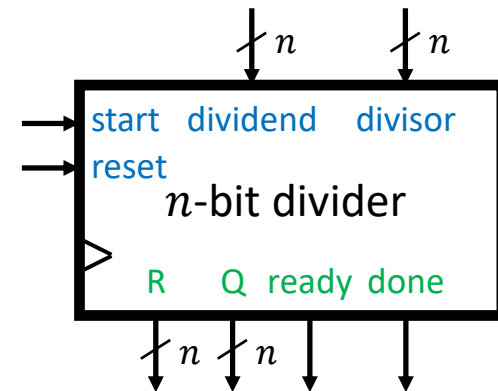- ❖ Fix your ASMD chart based on the divider circuit:





Arithmetic Mean Datapath

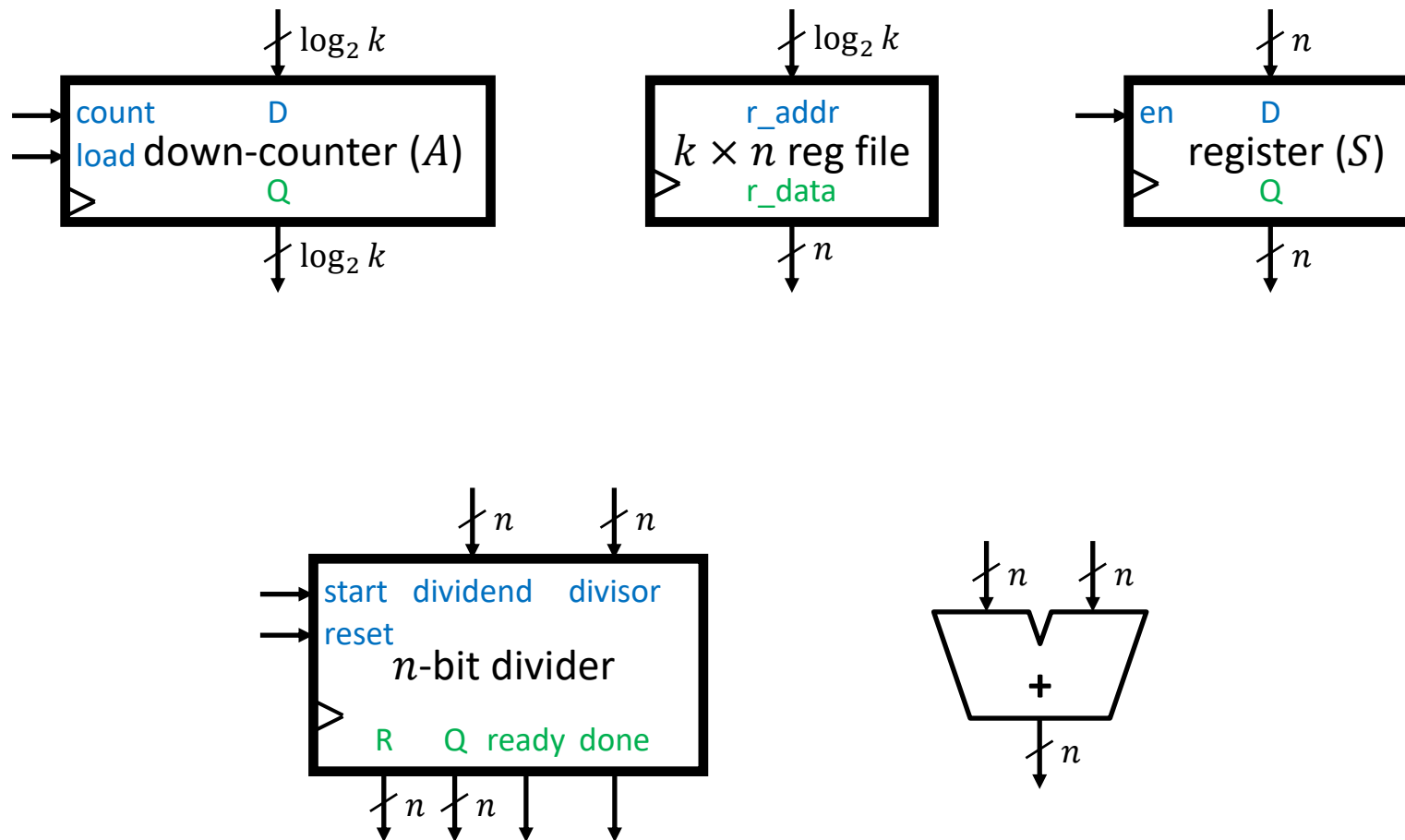

Technology Break

Aside: Load Loops

  
- ❖ For *some* initialization operations, you can get equivalent behavior from either the (1) outgoing edge or the (2) looping edge:



Aside: Start Loops

- ❖ What happens if we forget to de-assert *Start*?

- ❖ Fix:

 

Sorting Algorithm

- ❖ Design a circuit to sort k n -bit numbers stored in a set of registers in ascending order

Algorithm:

```
for i = 0 to k-2 do
  A = Reg[i]
  for j = i+1 to k-1 do
    B = Reg[j]
    if B < A then
      Reg[i] = B
      Reg[j] = A
      A = Reg[i]
    endif
  endfor
endfor
```

Example ($k = 4$):

| i | j | A | B | R[0] | R[1] | R[2] | R[3] |
|---|---|---|---|------|------|------|------|
| 0 | 1 | 3 | 7 | 3 | 7 | 1 | 0 |
| | | | | | | | |
| | | | | | | | |
| | | | | | | | |
| | | | | | | | |
| | | | | | | | |
| | | | | | | | |
| | | | | | | | |

Sorting Algorithm Specification

❖ Datapath

- A k -address *register file* (assume only 1 port)
- Two $\lceil \log_2(k) \rceil$ *up-counters* i and j
- Two registers A and B
- An n -bit *comparator* circuit to check for $B < A$

❖ Control

- Inputs *Start* and *Reset*, outputs *Ready* and *Done*
- Status signals:
- Control signals:

Sorting Algorithm Specification

❖ Datapath


- A k -address *register file* (assume only 1 port)
- Two $\lceil \log_2(k) \rceil$ *up-counters* i and j
- Two registers A and B
- An n -bit *comparator* circuit to check for $B < A$

❖ Timing Notes:


- RTL operations in a state occur on the *next* clock trigger
- Can $i \leftarrow x$ and $A \leftarrow \text{Reg}[i]$ be done simultaneously?
- Can $\text{Reg}[i] \leftarrow B$ and $\text{Reg}[j] \leftarrow A$ be done simultaneously?
- Swap operations *must* be done sequentially

Sorting Algorithm (ASMD Chart)


Sorting Algorithm Datapath

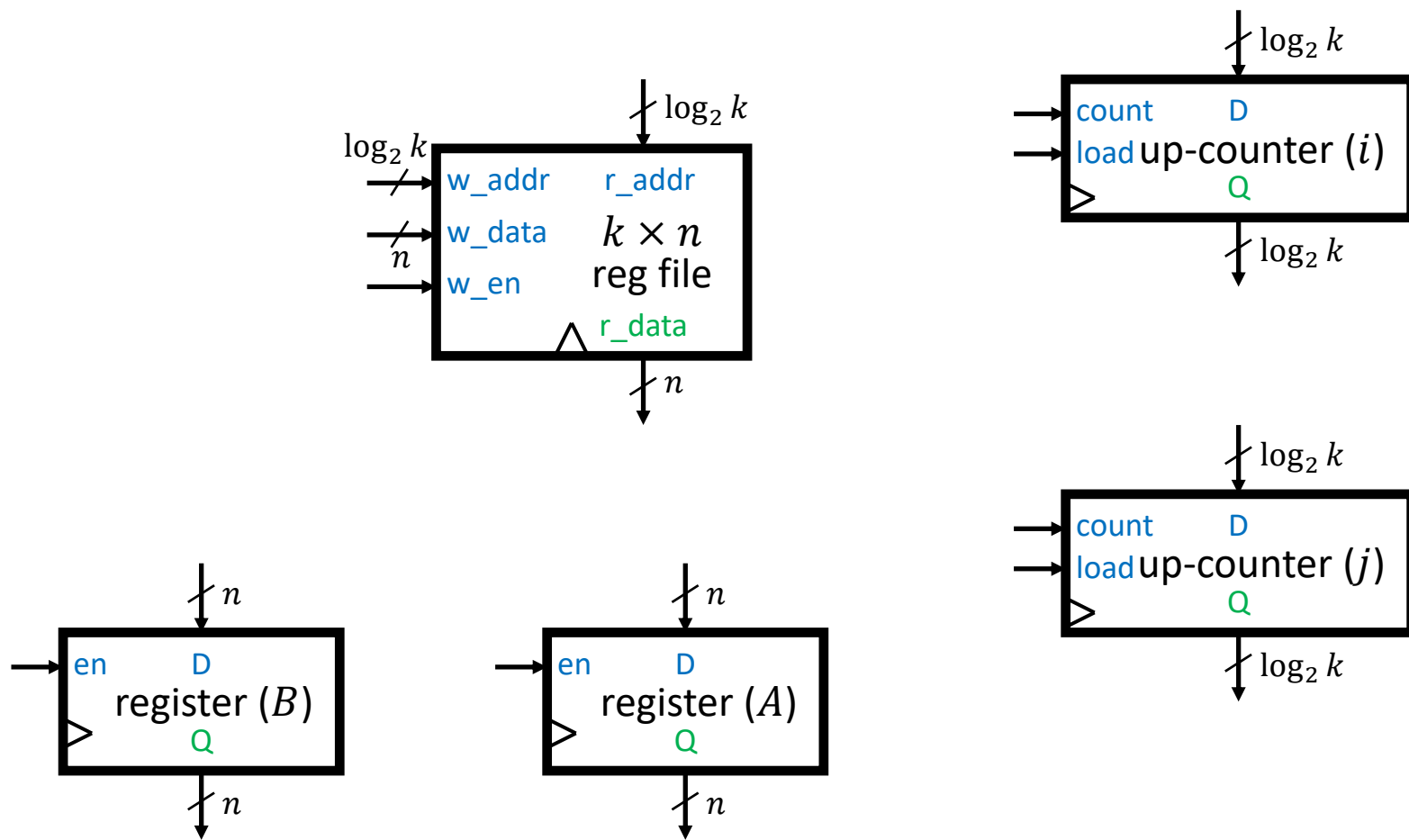

Alternate Sort Algorithm Datapath (1/2)

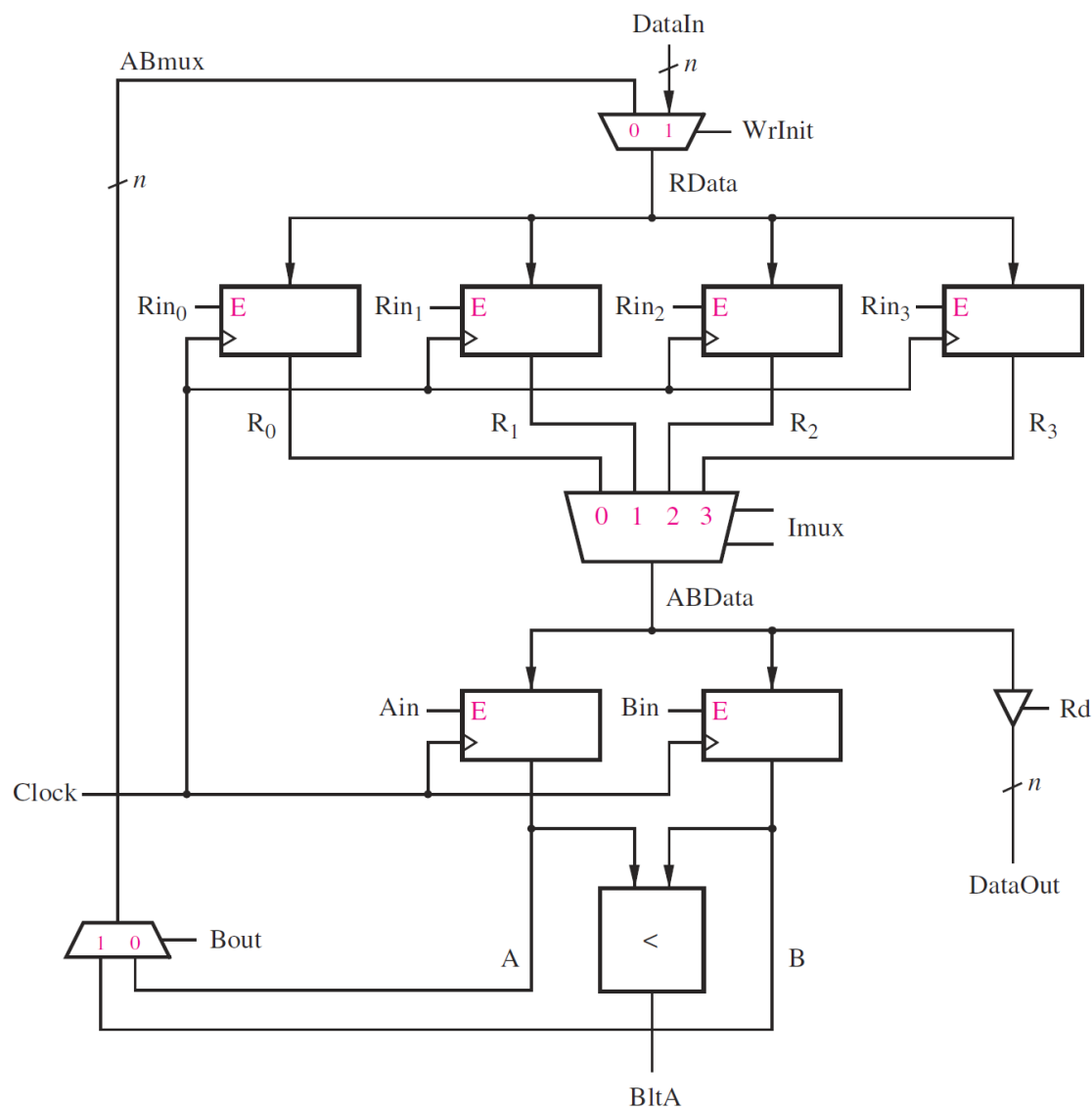

Alternate Sort Algorithm Datapath (2/2)

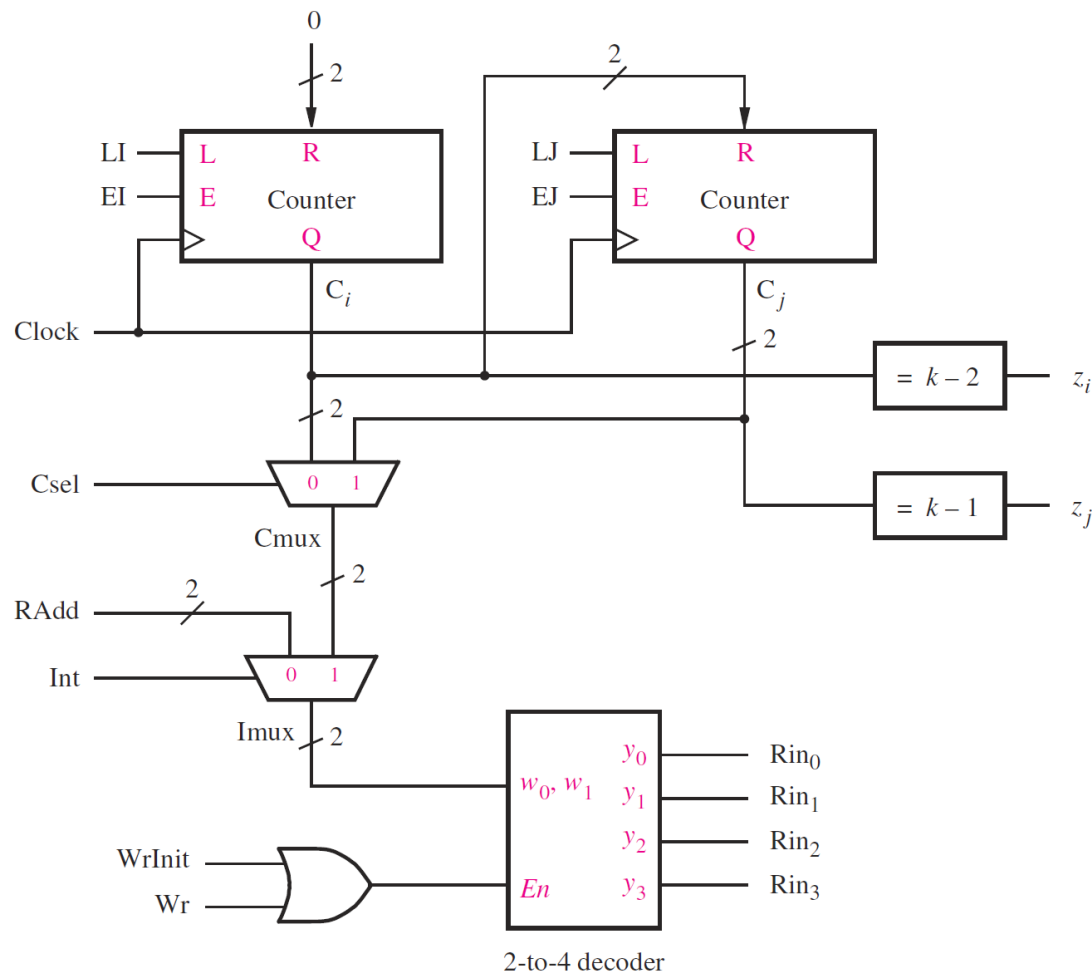

Lab 4 Preview: Binary Search

- ❖ Design a circuit that searches a *sorted* array for a given value by checking the middle element of the remaining portion of the array we would expect to find the given number:

```
L = 0
R = n - 1
while L <= R do
    m = floor((L + R)/2)
    if A[m] < T then
        L = m + 1
    else if A[m] > T then
        R = m - 1
    else
        return m
    endif
endwhile
return unsuccessful
```