

# Design of Digital Circuits and Systems

## Static Timing Analysis

**Instructor:** Justin Hsia

**Teaching Assistants:**

Colton Harris

Deepti Anoop

Gayathri Vadhyan

Jared Yoder

Lancelot Wathieu


Matthew Hung

# Relevant Course Information

- ❖ Lab 4 due Friday (5/3)
- ❖ Quiz 3 is this Thursday at **11:50** am (30 min)
  - ASM and ASMD charts
- ❖ Homework 5 (5/10) and Lab 5 (5/17) will be released on Thursday
  - Lab 5 is the longest “regular” lab, mostly because of debugging – careful with number representation
- ❖ Rest of course material will NOT show up in labs
 
# Review: Sequential Timing Constraints

- ❖ *Setup Time ( $t_s$  or  $t_{su}$ ):* how long the input must be stable before the CLK trigger for proper input read
- ❖ *Hold Time ( $t_h$ ):* how long the input must be stable after the CLK trigger for proper input read
- ❖ *"CLK-to-Q" Delay ( $t_{c2q}$  or  $t_{co}$ ):* how long it takes the output to change, measured from the CLK trigger




# When Can the Input Change?

- ❖ When a register input changes shouldn't violate hold time ( $t_h$ ) or setup time ( $t_{su}$ ) constraints within a clock period ( $T$ )
- ❖ Let  $t_{input,i}$  be the time it takes for the input of a register to change for the  $i$ -th time in a single clock cycle, measured from the CLK trigger:
  - Then we need  $t_h \leq t_{input,i} \leq T - t_{su}$  for all  $i$
  - Two separate constraints!

$$\textcircled{1} \quad t_{input,1} \geq t_h$$
 
$$\textcircled{2} \quad t_{input,n} \leq T - t_{su}$$




# Timing Constraint Questions

- 1) What are you solving for? Which constraint/inequality is relevant?
  - $t_h$  → hold time constraint
  - $t_{su}$  or  $T$  → setup time constraint
  - Combinational logic delay → “max” means setup time constraint, “min” means hold time constraint
- 2) Find the most relevant pathway to a register input
  - Hold time constraint → shortest pathway
  - Setup time constraint → longest pathway
- 3) Solve the inequality for chosen path using the given constants
 
# Practice Question

- Let  $T = 300$  ps,  
 $t_{su} = 80$  ps,  $t_h = 50$  ps,  
 $t_{CO} = 100$  ps.




- If In changes exactly on clock triggers, what are the limits on the XOR gate delay that ensure proper behavior?

$$0 + t_{xor} \geq t_h$$

$$t_{XOR} \in (50, 120) \text{ ps}$$

$$t_{co} + t_{xor} \leq T - t_{su}$$

 - Now let  $t_{XOR} = 100$  ps and In change a fixed  $t_{in}$  after each clock trigger, what ranges of  $t_{in}$  will result in proper behavior? Answer within a single clock cycle:




**BAD range**  
 $[300-80, 300+50]$  ← at Reg input  
 ↓ shift back by  $t_{xor}$   
 $[120, 250]$  ← at In

$$t_{in} \in [0, 120) \cup (250, 300] \text{ ps}$$


# What Affects Circuit Timing?
 
## ❖ A more realistic picture:

- **Logic depth of circuit pathways** } *part of design process*
- Length, resistance, and capacitance of wire } *baseline physical properties*
- Size of the transistors
- Operating conditions: Voltage & Temperature } *fluctuations based on conditions*




# Review: FPGA-Based Design Flow

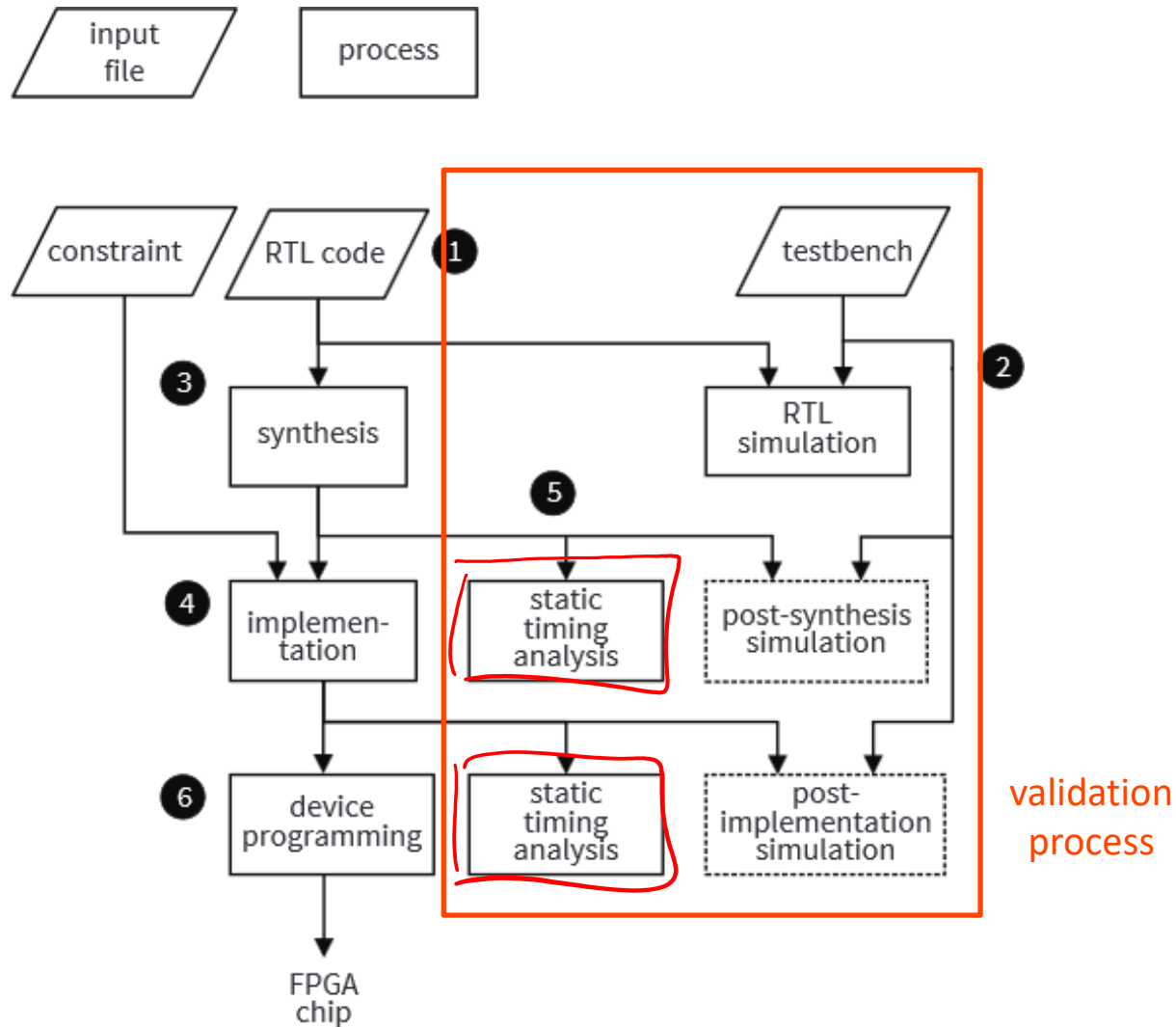

Source: Figure 2.3 from "FPGA Prototyping" by P. Chu




# Static Timing Analysis Flow

 

STA = Static Timing Analysis  
SDF = Standard Delay Format

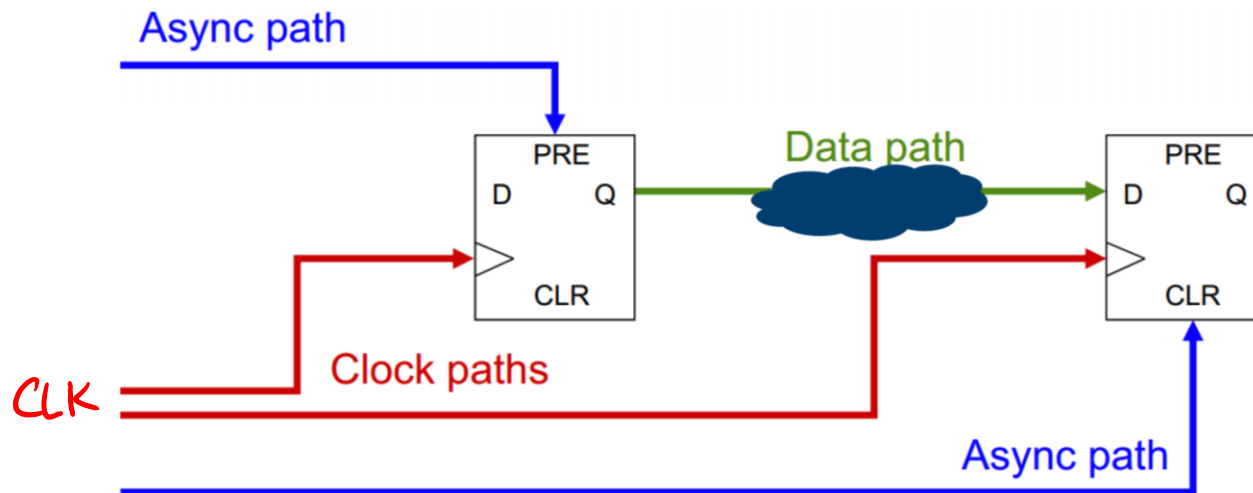
# Circuit Path Categorization

- ❖ **Data paths** are between inputs, sequential elements, and outputs
- ❖ **Clock paths** are from device ports or internally-generated clocks to the clock pins of sequential elements
- ❖ **Asynchronous paths** are between inputs and asynchronous set and clear pins of sequential elements



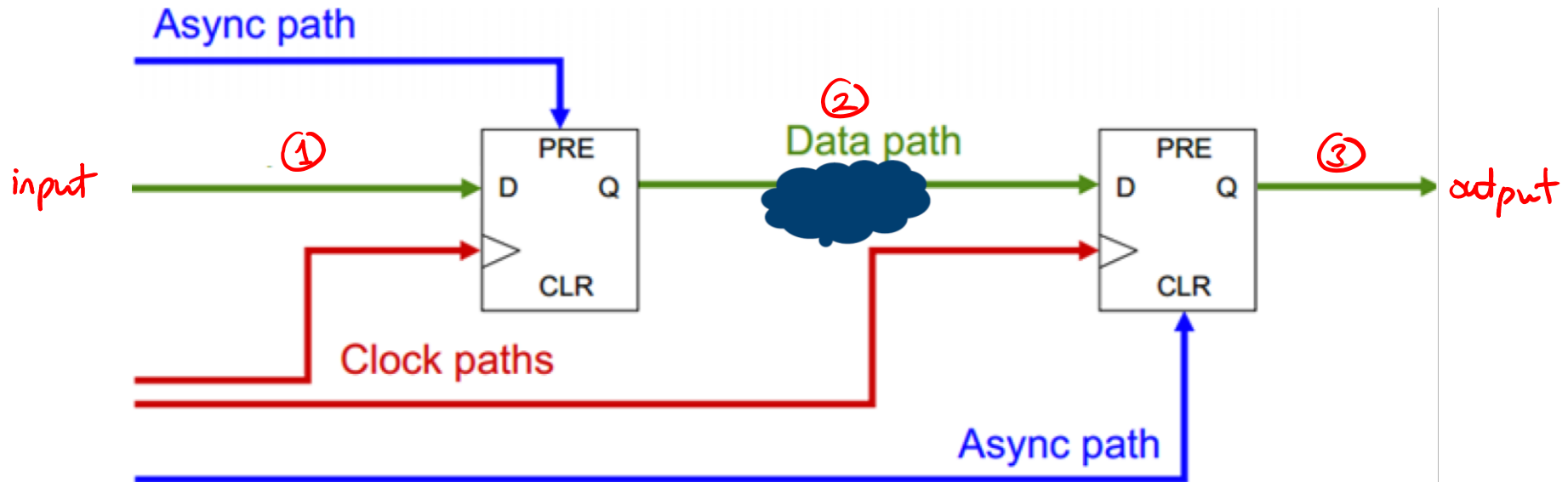
# Data Paths

- ❖ Three data path types:
  - 1) Input to sequential element
  - 2) Sequential element to sequential element
  - 3) Sequential element to output



 
# Data Path Validity

- ❖ A data signal is considered **valid** when it has finished computing and is stable
  - Note that this remains true until the next round of computation begins, which can cross clock cycle boundaries
- ❖ For proper behavior (*i.e.*, correct reads), the input to a register must remain valid throughout the setup and hold time constraints


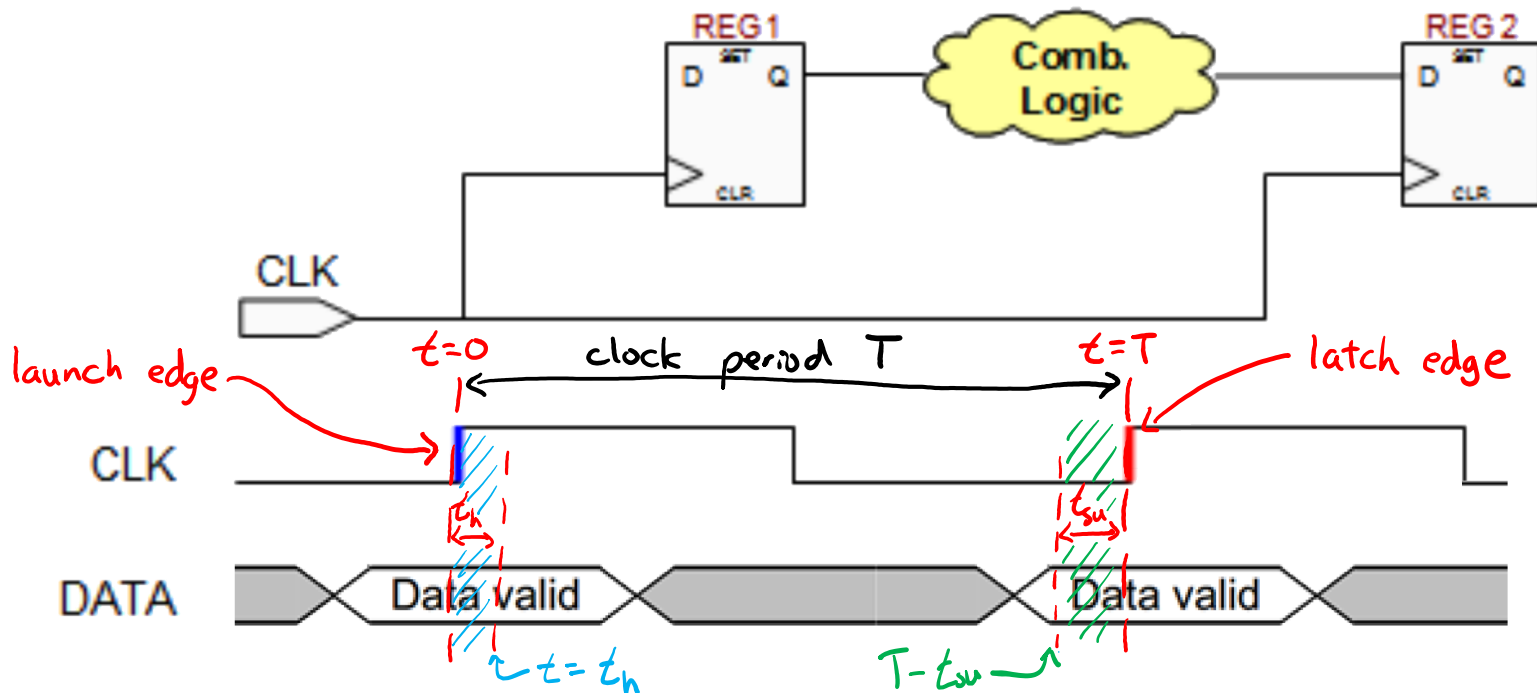
# Clock Edges

- ❖ Looking at a single clock cycle
  - **Launch Edge:** the clock edge that activates or *launches* the source register
  - **Latch Edge:** the clock edge that *latches* the data into the destination register




# Timing Delays and Points of Interest

- ❖ **Clock Network Delay ( $t_{clk}$ )**
  - How long it takes for changes in the clock signal to arrive at the register – the cause of *clock skew*
- ❖ **Clock-to-Q or Clock-to-out Delay ( $t_{C2Q}$ ,  $t_{CQ}$ , or  $t_{CO}$ )**
  - How long it takes the output to change, measured from the register's *received* clock edge – a property of the FF/register
- ❖ **Data Arrival Time (DAT)**
  - The time at which the destination register's input is settled
- ❖ **Clock Arrival Time (CAT)**
  - The time at which a clock edge arrives at the destination register

# Timing Delays and Points of Interest

DAT = data arrival time

CAT = clock arrival time

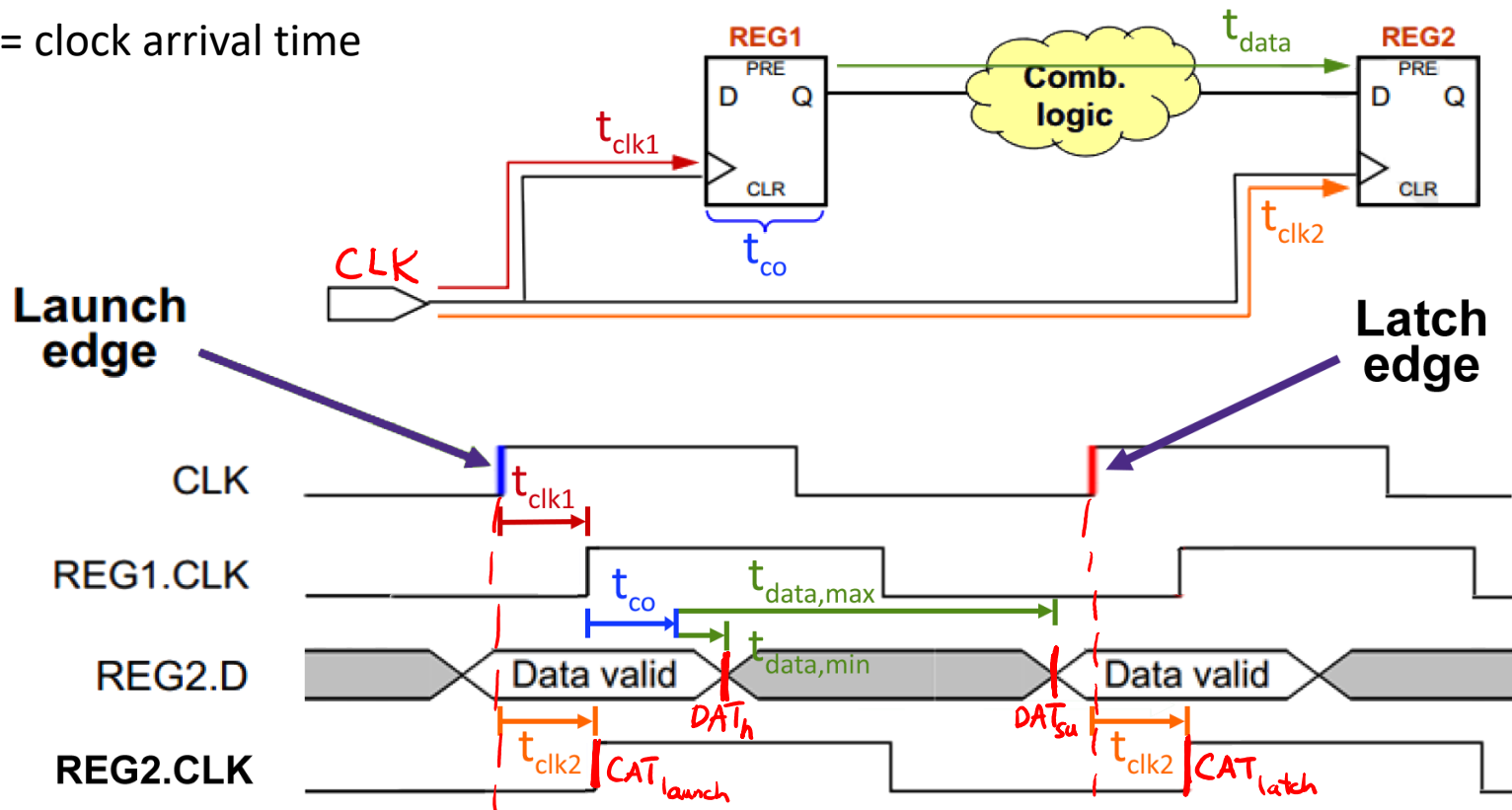


- $DAT_{su} = launch\ edge + t_{clk1,max} + t_{co,max} + t_{data,max}$
- $DAT_h = launch\ edge + t_{clk1,min} + t_{co,min} + t_{data,min}$
- $CAT_{latch/launch} = edge + t_{clk2}$

# Data Required Time (DRT)
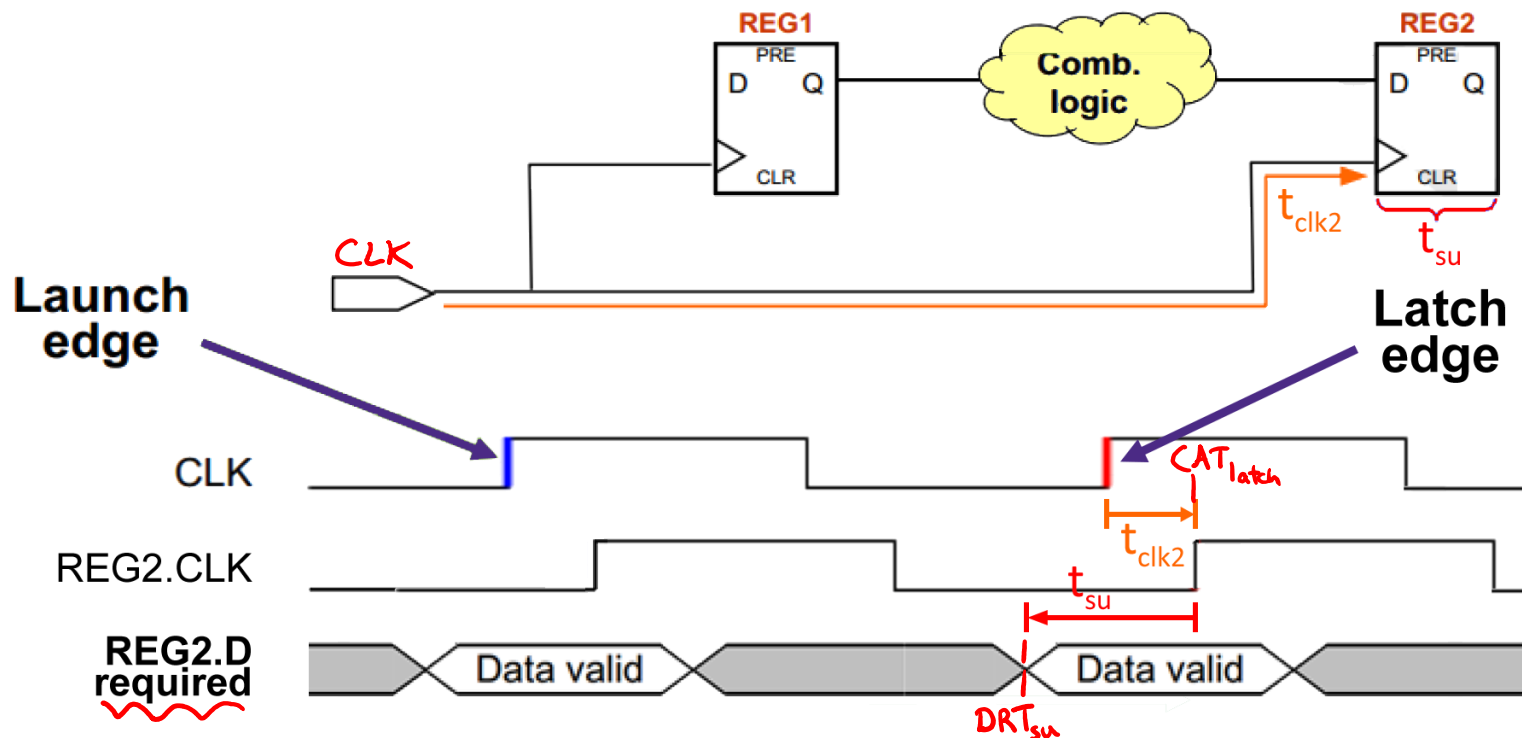
## ❖ Data Required Time for Setup ( $DRT_{su}$ )


- The minimum time required *before* the *latch* edge for data to get latched into the destination register
- **Clock Arrival Time<sub>latch</sub> – Setup Time**




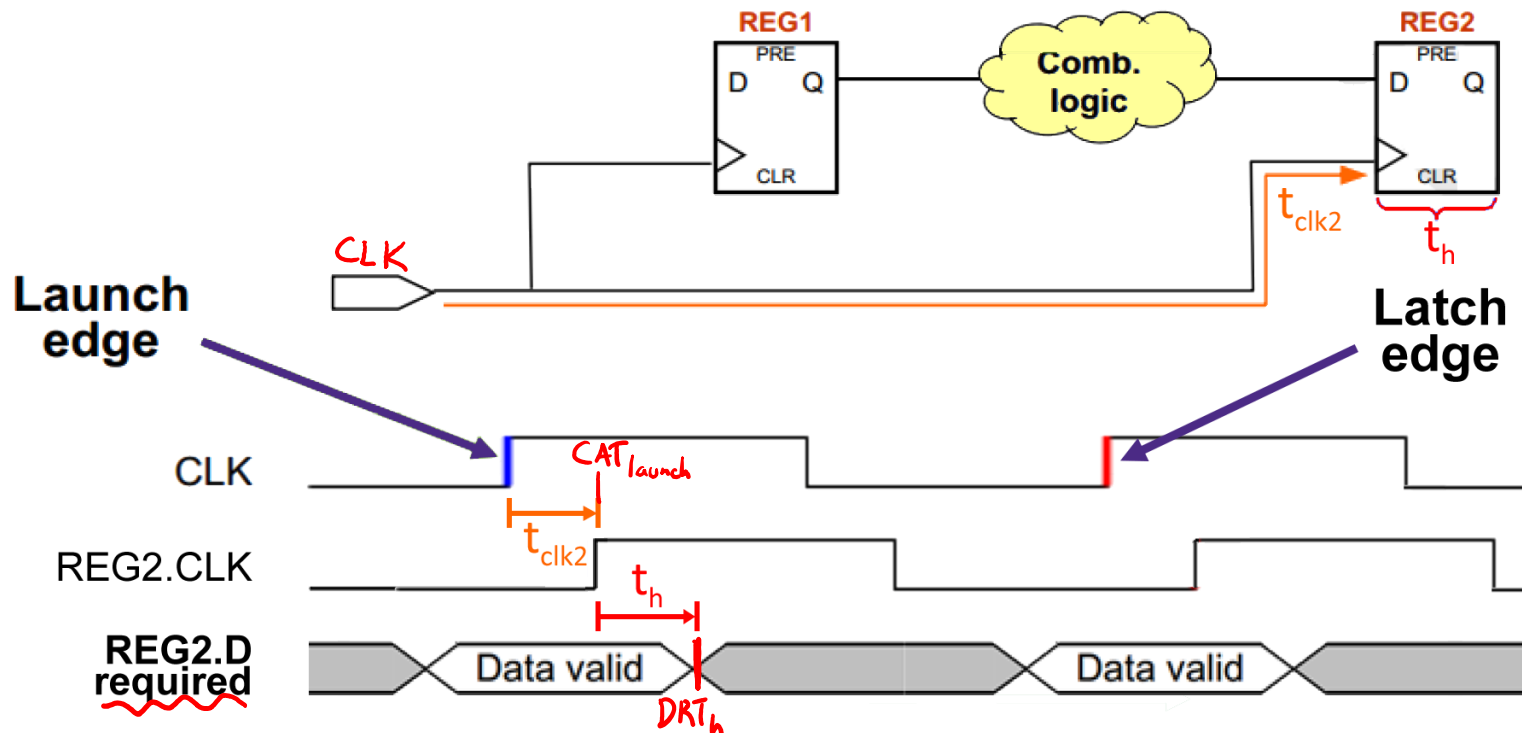
# Data Required Time (DRT)


- ❖ Data Required Time for Hold ( $DRT_h$ )
  - The minimum time required *after* the *launch* edge for the data to remain valid for successful latching
  - **Clock Arrival Time<sub>launch</sub> + Hold Time**


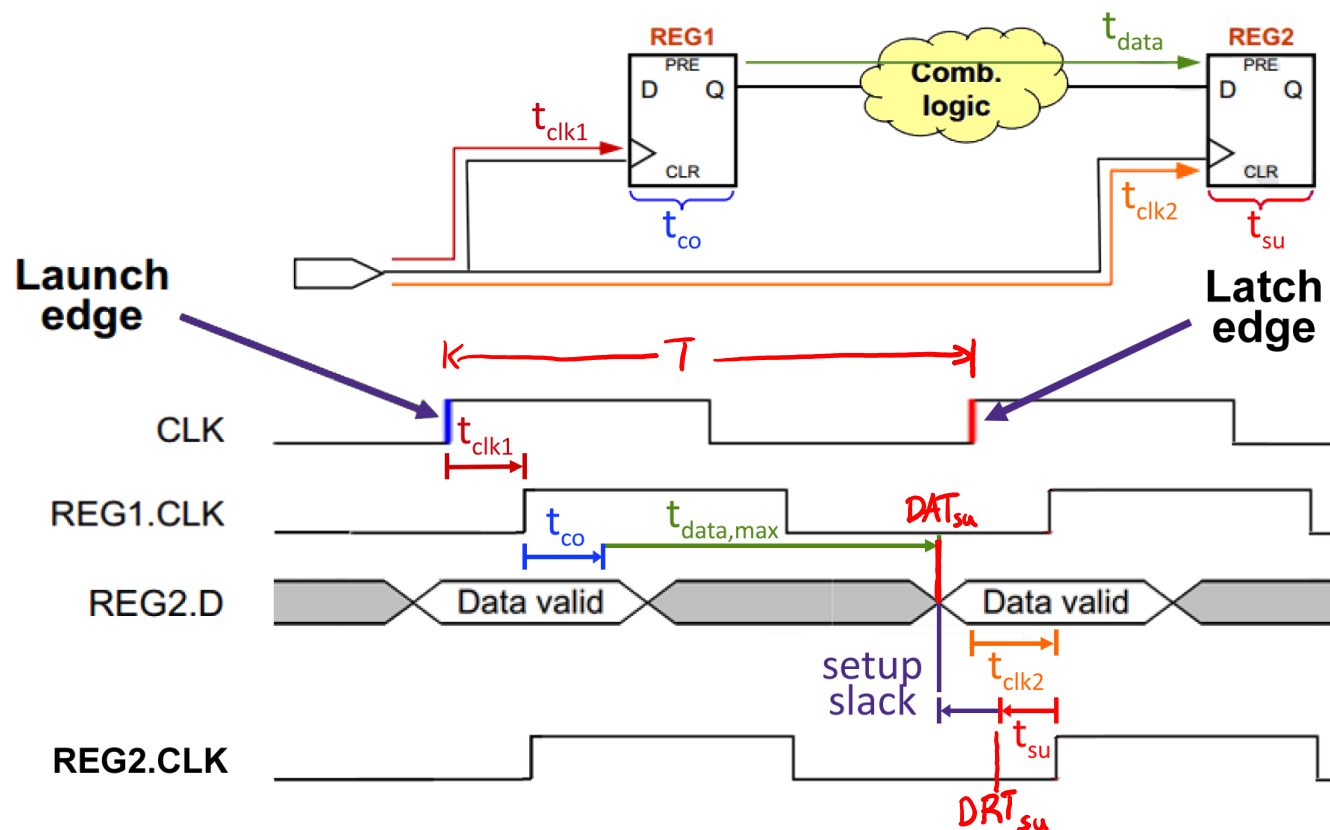
# Setup Slack

❖ Wiggle room for setup time violations


- Setup slack =  $DRT_{su} - DAT_{su}$ 
  - $T + t_{clk2} - t_{su}$  (points to  $DRT_{su}$ )
  - $t_{clk1} + t_{co} + t_{data,max}$  (points to  $DAT_{su}$ )
- Depends on clock frequency ( $T$ )





# Technology Break

# Setup Slack Example

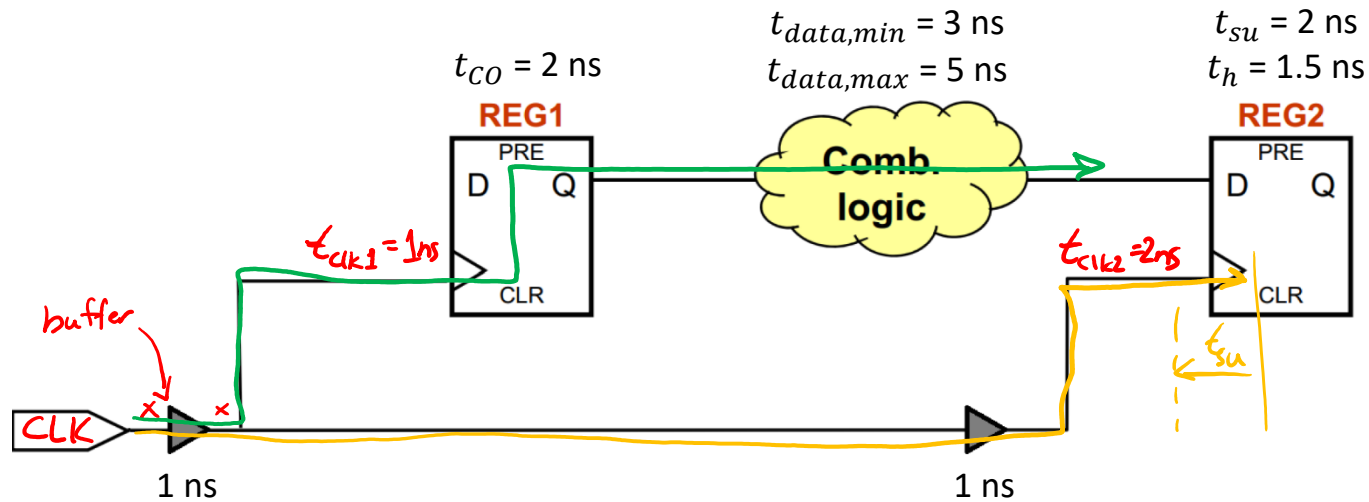


❖ Assume 100 MHz clock; clock period  $T = 10 \text{ ns}$

❖ Setup slack =  $DRT_{su} - DAT_{su}$

*latch edge*  
 $= \text{min clock path} - \text{max data path}$   
 $(T + t_{clk,2,min} - t_{su,max}) - (t_{clk,1,max} + t_{co,max} + t_{data,max})$   
 $(10 + 2 - 2) - (1 + 2 + 5)$

**setup slack = 2 ns**  $> 0$ , so no timing violation

# Hold Slack Example

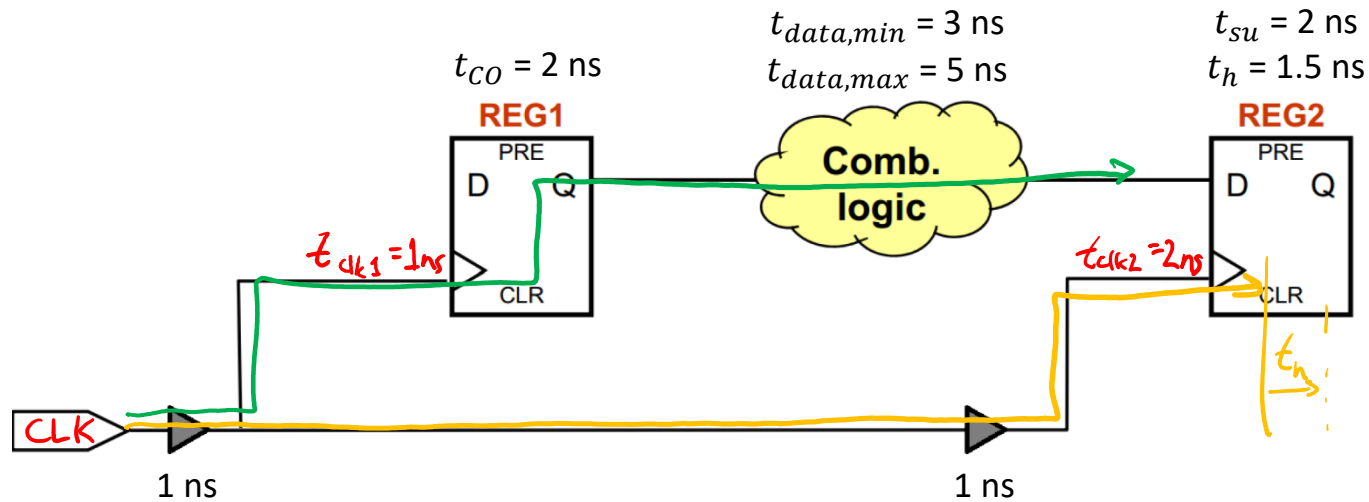

❖ Assume 100 MHz clock; clock period  $T = 10 \text{ ns}$


❖ Hold slack =  $DAT_h - DRT_h$

$= \text{min data path} - \text{max clock path}$   
 $(t_{clk1,min} + t_{CO,min} + t_{data,min}) - (0 + t_{clk2,max} + t_{H,max})$   
 $(1 + 2 + 3) - (2 + 1.5)$

hold slack = 2.5 ns

$> 0$ , so no timing violation

# Slack Example

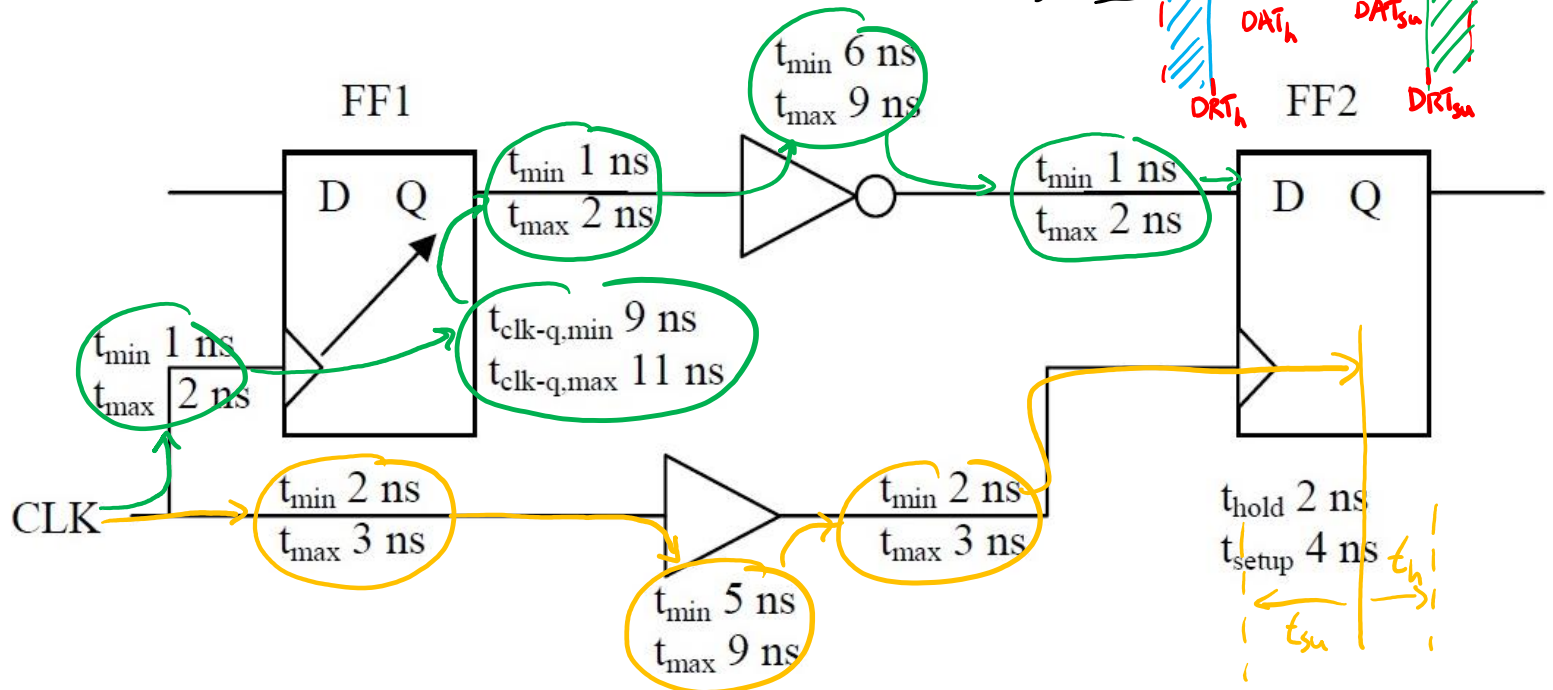

❖ Calculate the setup and hold slacks:

- Assume 50 MHz clock; clock period  $T = 20$  ns

- setup slack =  $\min \text{ clock path} - \max \text{ data path} = \boxed{-1 \text{ ns}}$


*(20 + 2 + 5 + 2 - 4) = 25      (2 + 11 + 2 + 9 + 2) = 26*

- hold slack =  $\min \text{ data path} - \max \text{ clock path} = \boxed{1 \text{ ns}}$

*(1 + 9 + 1 + 6 + 1) = 18      (3 + 9 + 3 + 2) = 17*

timing violation!

# Slack Example

 

- ❖ What is the fastest clock we can use with this circuit?

need setup slack  $\geq 0$  by changing clock speed/period ( $T$ )  
 so need  $T \geq 21 \text{ ns}$ , which means  $\frac{1}{T} \leq 47.6 \text{ MHz}$




# Synopsys Design Constraints (SDC)

- ❖ Synopsys Design Constraints describe timing constraints and exceptions
  - Quartus uses `.sdc` files to define clocks, I/O constraints, and other information that the fitter needs to make the best decisions
  - You can make and edit these using the TimeQuestGUI or by editing the `.sdc` file in a text editor (see hw5)
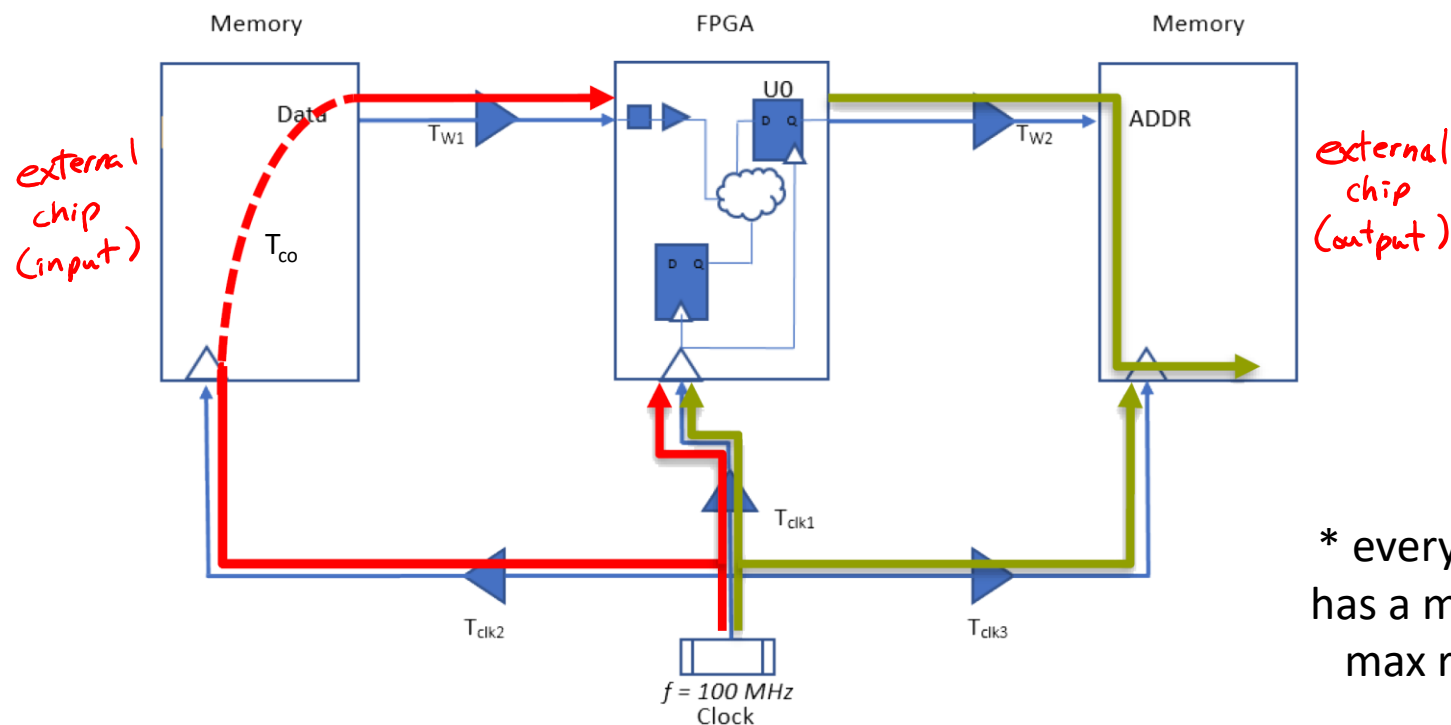
# I/O Constraints

- ❖ Let's examine the design constraints for the following example FPGA setup:
  - FPGA circuit between two external chips
  - $T_w$  are wire/board delays,  $T_{clk}$  are clock delays \*




\* every delay has a min and max range

# Input Delays
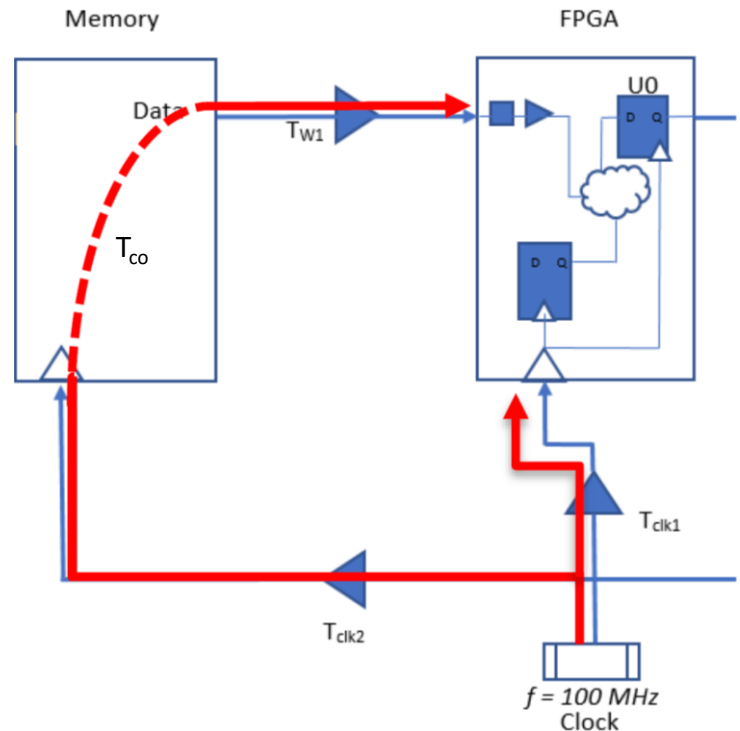
## ❖ set\_input\_delay

- Command to specify external delays feeding into the FPGA's input ports
- [https://www.intel.com/content/www/us/en/programmable/quartushelp/13.0/mergedProjects/tafs/tafs/tcl\\_pkg\\_sdc\\_ver\\_1.5\\_cmd\\_set\\_input\\_delay.htm](https://www.intel.com/content/www/us/en/programmable/quartushelp/13.0/mergedProjects/tafs/tafs/tcl_pkg_sdc_ver_1.5_cmd_set_input_delay.htm)



## ❖ Applied to this setup: *clock skew*


- $\text{input delay}_{\min} = \overbrace{(T_{\text{clk2},\min} - T_{\text{clk1},\max})}^{\text{clock skew}} + T_{\text{CO},\min} + T_{\text{W1},\min}$
- $\text{input delay}_{\max} = (T_{\text{clk2},\max} - T_{\text{clk1},\min}) + T_{\text{CO},\max} + T_{\text{W1},\max}$

# Output Delays
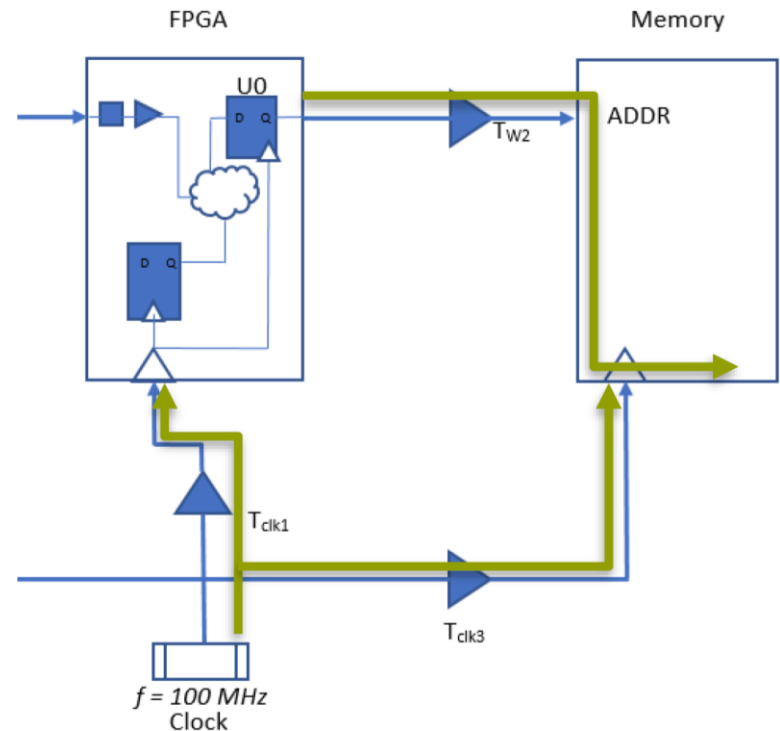
## ❖ set\_output\_delay

- Command to specify external delays leaving the FPGA's output ports

- [https://www.intel.com/content/www/us/en/programmable/quartushelp/13.0/mergedProjects/tafs/tafs/tcl\\_pkg\\_sdc\\_ver\\_1.5\\_cmd\\_set\\_output\\_delay.htm](https://www.intel.com/content/www/us/en/programmable/quartushelp/13.0/mergedProjects/tafs/tafs/tcl_pkg_sdc_ver_1.5_cmd_set_output_delay.htm)



## ❖ Applied to this setup: *clock skew*

- output delay<sub>min</sub> =  $(T_{clk1,min} - T_{clk3,max}) + T_{w2,min} - T_{h,max}$
- output delay<sub>max</sub> =  $(T_{clk1,max} - T_{clk3,min}) + T_{w2,max} + T_{su,max}$



# I/O Constraints

## ❖ Check the datasheet!

READ/WRITE CYCLE SWITCHING CHARACTERISTICS (Over Operating Range)						
Symbol	Parameter	-166		-133		Unit
		Min.	Max.	Min.	Max.	
f <sub>MAX</sub> <sup>(3)</sup>	Clock Frequency	—	166	—	133	MHz
t <sub>CC</sub> <sup>(3)</sup>	Cycle Time	6	—	7.5	—	ns
t <sub>KH</sub>	Clock High Time	2.4	—	2.8	—	ns
t <sub>KL</sub> <sup>(3)</sup>	Clock Low Time	2.4	—	2.8	—	ns
t <sub>CQ</sub> <sup>(3)</sup>	Clock Access Time	—	3.5	—	4	ns
t <sub>CQX</sub> <sup>(1)</sup>	Clock High to Output Invalid	3	—	3	—	ns
t <sub>CQLZ</sub> <sup>(1,2)</sup>	Clock High to Output Low-Z	0	—	0	—	ns
t <sub>CQHZ</sub> <sup>(1,2)</sup>	Clock High to Output High-Z	1.5	3.5	1.5	3.5	ns
t <sub>OEQ</sub> <sup>(3)</sup>	Output Enable to Output Valid	—	3.5	—	3.8	ns
t <sub>OEQX</sub> <sup>(1)</sup>	Output Disable to Output Invalid	0	—	0	—	ns
t <sub>OELZ</sub> <sup>(1,2)</sup>	Output Enable to Output Low-Z	0	—	0	—	ns
t <sub>OEHZ</sub> <sup>(1,2)</sup>	Output Disable to Output High-Z	2	4.5	2	5	ns
t <sub>AS</sub> <sup>(3)</sup>	Address Setup Time	2.1	—	2.1	—	ns
t <sub>SS</sub> <sup>(3)</sup>	Address Status Setup Time	1.5	—	1.5	—	ns
t <sub>WS</sub> <sup>(3)</sup>	Write Setup Time	1.5	—	1.5	—	ns
t <sub>CES</sub> <sup>(3)</sup>	Chip Enable Setup Time	1.5	—	1.5	—	ns
t <sub>AVS</sub> <sup>(3)</sup>	Address Advance Setup Time	1.5	—	1.5	—	ns
t <sub>AH</sub> <sup>(3)</sup>	Address Hold Time	1.0	—	1.0	—	ns
t <sub>SH</sub> <sup>(3)</sup>	Address Status Hold Time	0.5	—	0.5	—	ns
t <sub>WH</sub> <sup>(3)</sup>	Write Hold Time	0.5	—	0.5	—	ns
t <sub>CEH</sub> <sup>(3)</sup>	Chip Enable Hold Time	0.5	—	0.5	—	ns
t <sub>AVH</sub> <sup>(3)</sup>	Address Advance Hold Time	0.5	—	0.5	—	ns

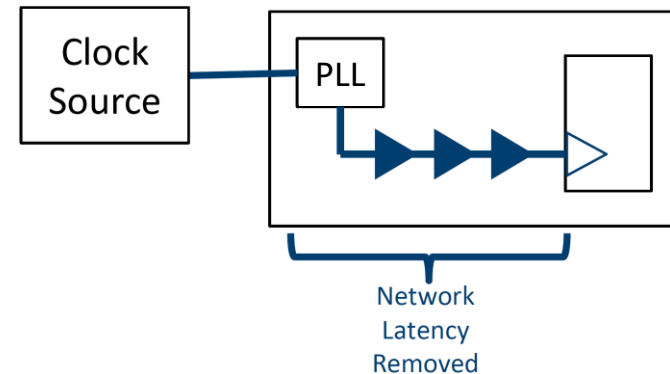 
# Clock Effects

- ❖ **Clock Latency:** delay for clock signal to reach components
  - Source latency: the delay between the clock definition and its source
  - Network latency: the delay between the clock definition and register clock pins
    - [extra] Often dealt with using an onboard phase-locked loop (PLL) – see `derive_pll_clocks` command


 
# Clock Effects

- ❖ **Clock Uncertainty:** clock signal does not arrive at every clock pin simultaneously
  - Skew: differences in arrival time of a clock signal to different components
  - Jitter: deviations from defined period
  - Synchronous clock domain crossings (future lecture)



# Timing Closure

- ❖ Timing constraints need to be met *simultaneously*
  - Sometimes fixing one violation will introduce another
- ❖ Fixing **hold violations**: caused by fast data path and destination register's clock latency
  - Add delay in the data path with buffers or pairs of inverters (done automatically by Quartus)
- ❖ Fixing **setup violations**: data arrives too late compared to the destination register's clock speed
  - Slow down the clock (undesirable)
  - Tell fitter to try harder or confine logic to a smaller area
  - Rewrite code to simplify logic
  - Add *pipelining* (next lecture)