

High-speed signaling

- ◆ Delays
- ◆ Transmission lines
- ◆ Ringing and terminations
- ◆ Pin inductance
- ◆ Tips and suggestions

What does high-speed
mean?

Abstractions in digital design

- 1 Digital interpretation of analog values
 - ⇒ Transistors as switches
 - ⇒ Analog voltages as "1s" or "0s"
- 2 Logic devices as idealized Boolean primitives
 - ⇒ Switches as logic elements
 - ⇒ Ignore electrical characteristics of devices, wire, etc.
- 3 Steady-state abstraction
 - ⇒ Combinational: Outputs depend on inputs *after a sufficient time*
 - ⇒ Sequential: Outputs retain their *settled state*
 - ▶ Clock hides transient behavior
- 4 Finite-state behavior of sequential systems



Definition of “high speed”

The speed at which one or more digital abstractions fail, as a direct consequence of the circuit speed

- ⇒ Speed \equiv Clock frequency and/or edge rates
- ⇒ Typical problems
 - ◆ Logic gates or flip-flops don't have time to settle
 - ◆ Clock skew causes races
 - ◆ Wire (interconnect) acts like transmission lines



When wire isn't...

  - ◆ **All** wires are transmission lines
 - ⇒ Just like all voltages are analog
- ◆ Past: Signals on PCBs were slow
 - ⇒ Wire delays were small compared with signal risetimes
 - ⇒ Wires passed digital voltages unchanged
- ◆ Today: PCB design **requires** transmission-line analysis
 - ⇒ Wire delays are long compared with signal risetimes
 - ⇒ Wires don't pass digital voltages unchanged



Horizontal Scale = 20 ns/cm

Background: Time constants

 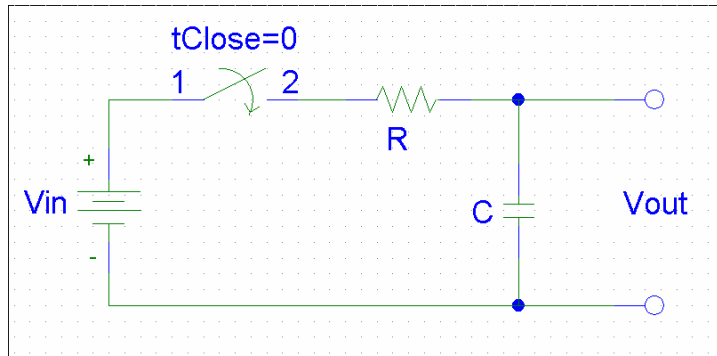

$$V_{in} = v_r + V_{out} \quad v_r = iR \quad i = C \frac{dV_{out}}{dt}$$

$$V_{in} = iR + V_{out}$$

$$V_{in} = RC \frac{dV_{out}}{dt} + V_{out}$$

$$-RC dV_{out} = (V_{out} - V_{in}) dt$$

$$-\frac{dt}{RC} = \frac{dV_{out}}{(V_{out} - V_{in})}$$


$$-\frac{1}{RC} \int_0^t dt = \int_0^{v_{out}(t)} \frac{dV_{out}}{(V_{out} - V_{in})}$$

$$-\frac{t}{RC} = \ln(V_{out}(t) - V_{in}) - \ln(-V_{in})$$

$$V_{out}(t) = V_{in} \left(1 - e^{-\frac{t}{RC}} \right)$$

Background: Maximum power transfer

 - ◆ How much power do you transfer to R_L ?
 - ⇒ Transfer zero power when $R_L = 0$
 - ⇒ Transfer zero power when $R_L = \infty$
 - ⇒ Transfer maximum power when $R_L = R_S$




- ◆ Our problem: R_S is a transmission line (a wire)
 - ⇒ Transfer maximum power when $R_L =$ wire impedance
 - ⇒ Else some power is returned to the voltage source

Transmission-line model

- ◆ This is a model of a wire (an abstraction)
 - ⇒ Adequate when dispersion is low

 
Equivalent Circuit of a Transmission Line



◆ Cases

- | | |
|-------------------------------|----------------------------------|
| 1) R_o, C_o, L_o are small: | Treat wire as ideal |
| 2) R_o, L_o are small: | Treat wire as lumped capacitance |
| 3) L_o is small: | Treat wire as distributed RC |
| 4) None are small: | Treat wire as transmission line |

Cases 2, 3: RC models

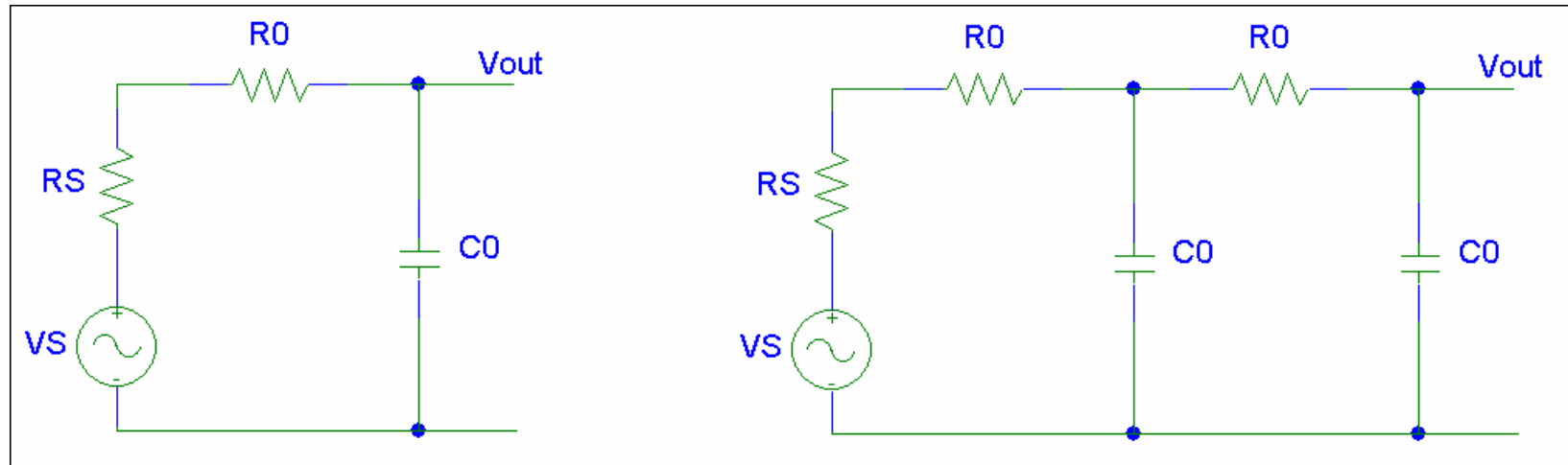

$$R_0 \ll R_S$$

$$V_{\text{out}} = 1 - e^{-t/RC}$$

Where R is the total resistance
 C is the total capacitance
 Wire is short (defined later)

$$R_0 \sim R_S$$

$$V_{\text{out}} = 1 - e^{-2t/R_0 C_0 \ell^2}$$

Where ℓ is the length of the wire
 R0 is resistance per unit length
 C0 is capacitance per unit length
 R0 dominates inductance L

Case 4: Transmission-line model

- ◆ Problem: Signal risetime is faster than the wire delay
 - ⇒ Inductance L limits the propagation velocity by $V=L(dI/dt)$
- ◆ Thought process: We won't see ringing if it occurs entirely during the signal's rising or falling edge

- ◆ Assume a simple wire

- ⇒ Require $\text{length}_{\max} < \frac{t_r}{2t_{pd}}$ or $\text{delay}_{\max} < \frac{t_r}{2}$

- ⇒ Where $t_r \equiv$ rise time
- ⇒ $t_{pd} \equiv$ delay per unit length
- ⇒ length \equiv length of wire
- ⇒ delay \equiv wire delay = $t_{pd} \times$ length

The factor of 2 accounts for the fact that the signal has to travel to the end of the wire, then return on the ground plane

Some definitions

◆ $t_{pd} = \sqrt{L_0 C_0}$ in ns/ft

⇒ The signal propagation time

◆ $Z_0 = \sqrt{\frac{L_0}{C_0}}$ in Ohms

⇒ The impedance of a transmission line

◆ How to find C_0 and L_0 ?

- ⇒ Use an LCR meter
- ⇒ Use an EM simulator

L_0 is inductance per unit length

C_0 is capacitance per unit length


Most PCB vendors will size traces for you

You just tell them Z_0

Microstrip: Wire over a plane

$$Z_0 = \frac{87}{\sqrt{\epsilon_r + 1.41}} \ln \left(\frac{5.98h}{0.8w + t} \right) \text{ Ohms}$$
 
$$t_{pd} = 1.017 \sqrt{0.475\epsilon_r + 0.67} \text{ ns/ft}$$




ϵ_r is a relative dielectric constant (ref to vacuum)

Example: $\epsilon_r = 4.8$ for FR-4 epoxy-glass

Stripline: Wire sandwiched between planes

$$Z_0 = \frac{60}{\sqrt{\epsilon_r}} \ln \left(\frac{4b}{0.67\pi w \left(0.8 + \frac{t}{w} \right)} \right) \quad \text{Ohms}$$
 
$$t_{pd} = 1.017 \sqrt{\epsilon_r} \quad \text{ns/ft}$$



Tip: Planes can be power *or* ground

Loading a line

- ◆ Attaching logic gates to a line increases the capacitance
 - ⇒ Where $C_d \equiv$ Capacitive load on transmission line

$$Z'_0 = \frac{Z_0}{\sqrt{1 + \frac{C_d}{C_0}}}$$

$$t'_{pd} = t_{pd} \sqrt{1 + \frac{C_d}{C_0}}$$



What if we violate the limit?

- ◆ Get overshoot/undershoot and reflections
 - ⇒ Signal bounces back and forth between the ends of the line
 - ⇒ Bounce gets reduced by a factor ρ at each reflection

$$\rho_S = \frac{R_S - Z_0}{R_S + Z_0}$$

$$\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$$

Fig. 4-3 Multiple Reflections Due to Mismatch at Load and Source

  

H = 20 ns/div
V = 0.5 V/div

Terminating transmission lines: Option1

- ◆ Terminate line into an equivalent load

- ⇒ Advantages

- ◆ Can distribute gates along line


- ⇒ Disadvantages

- ◆ Driver consumes lots of power


- ◆ Driver has large output currents

- ◆ Driver has large transients

 - ◆ Note: Properly terminated lines look like purely resistive loads



(a) Test Configuration

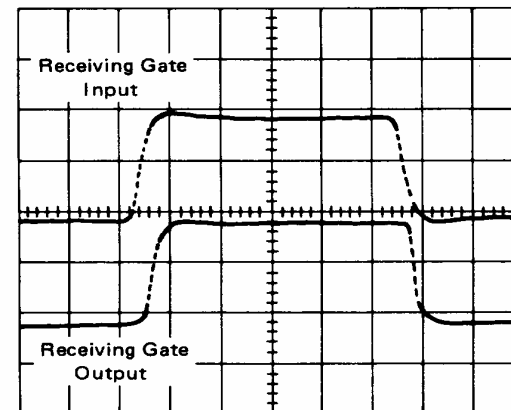


Horizontal Scale = 10 ns/cm

(b) Input and Output Waveforms

Terminating transmission lines: Option2

- ◆ Terminate the line into a Thevenin equivalent load

 - ⇒ Termination as good as option1
- ⇒ Advantages
 - ◆ Can distribute gates along line
 - ◆ Smaller peak output current than option1
 - ◆ Smaller driver transients than option1
- ⇒ Disadvantages
 - ◆ Same total power as option1
 - ◆ Need to set DC bias at logic threshold



$$R_L = \frac{R_1 R_2}{R_1 + R_2}$$



Terminating transmission lines: Option3

◆ Series terminate the line

- ⇒ Termination inferior to option1
- ⇒ Advantages
 - ◆ No static power consumption
 - ◆ Can drive many loads
- ⇒ Disadvantages
 - ◆ Half-amplitude transients on line
 - ◆ Cannot place gates along line (only place gates at ends)

Tip: $Z_{\text{wire}} \sim 100\text{--}140$ Ohms
(assuming no ground plane)


Fig. 4-7 Series Terminated Line and Waveforms

  

H = 10 ns/div
V = 0.4 V/div

Driving multiple loads using option3


Parallel Fanout Using Series Termination

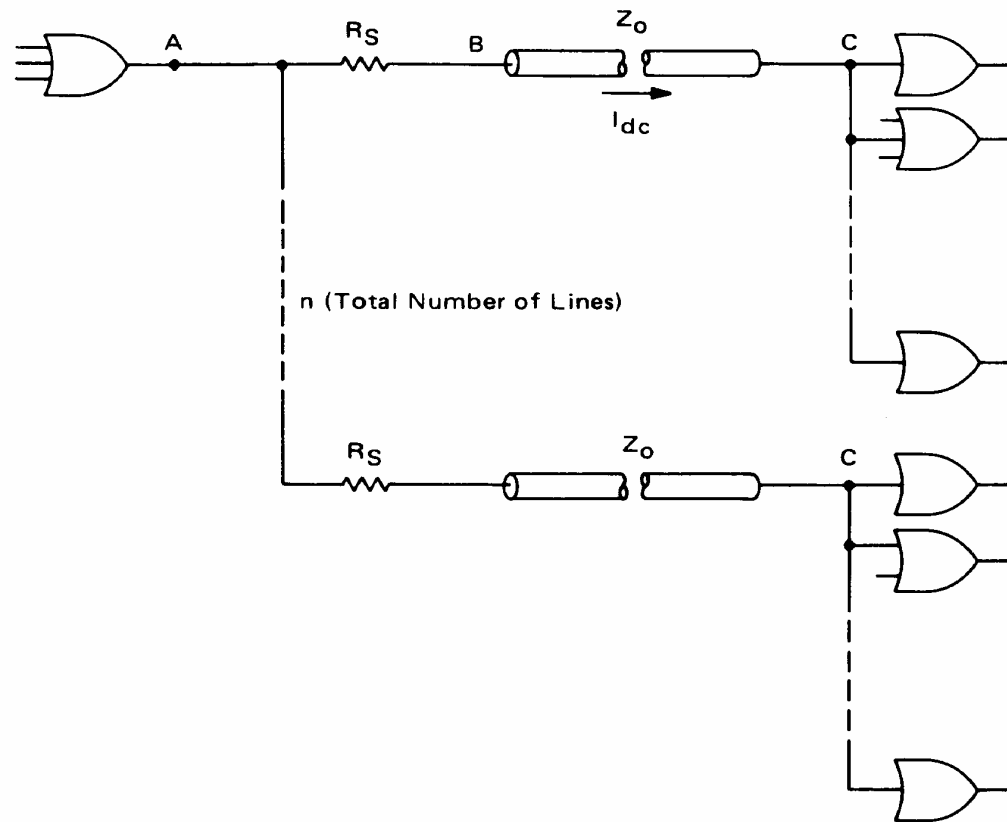

Terminating transmission lines: Option4

- ◆ Differentially terminate the line

 - ⇒ Termination as good as option1
- ⇒ Advantages
 - ◆ Can distribute gates along line
 - ◆ Differential signals
 - ◆ Low crosstalk
 - ◆ Don't need contiguous ground plane
- ⇒ Disadvantages
 - ◆ High driver power
 - ◆ Need differential receivers



- ◆ Note: Great for buses

- ⇒ Put terminations at both ends of bus
- ⇒ SCSI uses this approach

Issues

- ◆ Rule was: $\text{length}_{\text{max}} < \frac{t_r}{2t_{\text{pd}}}$ or $\text{delay}_{\text{max}} < \frac{t_r}{2}$
- ◆ But...
 - ⇒ Series terminated lines have accelerated rise times
 - ◆ Voltage doubles at line end
 - ⇒ Analysis shows 15% overshoot/undershoot
 - ◆ Assumes accurate calculations...
- ◆ Instructor experience: **This rule is not conservative enough**

A more conservative rule

◆ **Rule:** $\text{length}_{\max} < \frac{t_r}{4t_{pd}}$ or $\text{delay}_{\max} < \frac{t_r}{4}$

- ⇒ Where $t_r \equiv$ rise time
- ⇒ $t_{pd} \equiv$ delay per unit length
- ⇒ length \equiv length of wire
- ⇒ delay \equiv wire delay = $t_{pd} \times \text{length}$
- ⇒ Use t'_{pd} when line is loaded

Back of the envelope calculations

◆ Estimate the wire delay in ns

- ⇒ Twisted pair: ~ 8.5 in/ns
 - ⇒ Coaxial cable: ~ 8 in/ns
 - ⇒ Microstrip: ~ 7 in/ns
 - ⇒ Stripline: ~ 5.5 in/ns
- Assuming FR-4

◆ Check if the wire is short

- ⇒ delay $< \frac{t_r}{4}$???
- ⇒ If yes, wire will act like wire
 - ◆ You are safe
- ⇒ If no, wire **may** act like a transmission line
 - ◆ Do more analysis


Example:
1ns risetime
5in trace over gnd

Delay = $5/7$ ns
 $t_r/4 = 1/4$ ns

$5/7 > 1/4$
⇒ You are not safe

Tip: Pin inductance and I/O speed

 - ◆ Rule of thumb: $t_{r_min} > \frac{5L}{Z_0}$
 - ⇒ t_{r_min} is minimum signal rise time
 - ⇒ L is pin inductance
 - ⇒ Z_0 is trace impedance
 - ⇒ Example:
 - ▶ $L = 5\text{nH}$
 - ▶ $Z_0 = 50\text{ Ohms}$
 - ▶ $t_{r_min} = 500\text{psec}$



Tips for series terminations

- ◆ Use a series resistor for each load
 - ⇒ Drive all loads in parallel
- ◆ Do not daisy-chain loads
 - ⇒ Half-amplitude voltage swings on the wire
- ◆ Reduce R_s by 33%
 - ⇒ Example: If $Z=50$, choose $R_s = 33$ Ohms
 - ◆ Driver has a finite source impedance
 - ◆ Line loads cause $Z \downarrow$
 - ◆ Slight overshoot is good (fast edges)

Tips for minimizing reflections

- ◆ Reduce signal rise times
 - ⇒ Example: Xilinx has selectable output rise times
- ◆ Reduce line lengths
- ◆ Terminate long lines properly
- ◆ Use contiguous ground or power planes
 - ⇒ Under transmission lines
 - ⇒ Or use differential terminations
- ◆ Avoid sharp bends in wires
 - ⇒ Curves are better than corners

Tips for routing traces on PCBs

- ◆ Use differential wires to communicate between systems
 - ⇒ Or through card-edge connectors
- ◆ Use ground & power planes
 - ⇒ Low-Q decoupling capacitors between them
 - ⇒ Avoid cuts in ground plane
 - ◆ esp. under controlled-impedance traces
- ◆ Avoid long parallel wires
 - ⇒ Unless they are differential
 - ⇒ Using ground between traces reduces crosstalk

Tips for ground planes

- ◆ The width of a ground plane must be $3\times$ the width of the controlled impedance trace
 - ⇒ Do not put cuts in the ground plane
 - ⇒ Put ground plane directly under trace

