

# Sequential Logic


- Verilog uses certain idioms to describe latches, flip-flops and FSMs
- Other coding styles may simulate correctly but produce incorrect hardware

# D Flip-Flop

```
module flop(input          clk,
            input    [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <= d;                // pronounced "q gets d"

endmodule
```

 

**Any signal assigned in an `always` statement must be declared `reg`.** In this case `q` is declared as `reg`


***Beware:*** A variable declared `reg` is not necessarily a registered output.

We will show examples of this later.

Note the use of the `<=` assignment operator

 
# Resettable D Flip-Flop

```
module flopr(input          clk,  
            input          reset,  
            input  [3:0]  d,  
            output reg [3:0] q);  
  
    // synchronous reset  
    always @ (posedge clk)  
        if (reset) q <= 4'b0;  
        else      q <= d;  
  
endmodule
```


 
# Resettable D Flip-Flop

```
module flopr(input          clk,  
            input          reset,  
            input  [3:0] d,  
            output reg [3:0] q);  
  
    // asynchronous reset  
    always @ (posedge clk, posedge reset)  
        if (reset) q <= 4'b0;  
        else      q <= d;  
  
endmodule
```




# D Flip-Flop with Enable

```
module flopren(input          clk,
               input          reset,
               input          en,
               input [3:0]    d,
               output reg [3:0] q);


// asynchronous reset and enable
always @ (posedge clk, posedge reset)
    if (reset) q <= 4'b0;
    else if (en) q <= d;

endmodule
```

 
 
# Latch

```
module latch(input          clk,  
             input    [3:0] d,  
             output reg [3:0] q);  
  
    always @ (clk, d)  
        if (clk) q <= d;  
  
endmodule
```



**Warning:** We won't use latches in this course, but you might write code that inadvertently implies a latch. So if your synthesized hardware has latches in it, this indicates an error.

# 8-bit Register with Synchronous Reset

```
module reg8
  (input reset,
   input CLK,
   input [7:0] D,
   output reg [7:0] Q);

  always @(posedge CLK)
    if (reset)
      Q <= 0;
    else
      Q <= D;
endmodule // reg8
```

# N-bit Register with Asynchronous Reset

```
module regN
  #(parameter N=8)
  (input reset,
   input CLK,
   input [N-1:0] D,
   output reg [N-1:0] Q);

  always @(posedge CLK or posedge reset)
    if (reset)
      Q <= 0;
    else if (CLK == 1)
      Q <= D;
endmodule // regN
```



# Shift Register Example

```
// 8-bit register can be cleared, loaded, shifted left
// Retains value if no control signal is asserted

module shiftReg
  (input CLK,
   input clr,           // clear register
   input shift,        // shift
   input ld,           // load register from Din
   input [7:0] Din,    // Data input for load
   input SI,           // Input bit to shift in
   output reg [7:0] Dout);

  always @(posedge CLK) begin
    if (clr)           Dout <= 0;
    else if (ld)       Dout <= Din;
    else if (shift)    Dout <= { Dout[6:0], SI };
  end

endmodule              // shiftReg
```



# Counter Example

- Simple components with a register and extra computation
  - Customized interface and behavior, e.g.
    - counters
    - shift registers

```
// 8-bit counter with clear and count enable controls
module count8
  (input          CLK,
   input          clr, // clear counter
   input          cntEn, // enable count
   output reg [7:0] Dout); // counter value

  always @(posedge CLK)
    if (clr)          Dout <= 0;
    else if (cntEn)   Dout <= Dout + 1;

endmodule
```



# Rules for Signal Assignment

- Use `always @ (posedge clk)` and nonblocking assignments (`<=>`) to model synchronous sequential logic

```
always @ (posedge clk)
    q <= d; // nonblocking
```

- Use continuous assignments (`assign ...`) to model simple combinational logic.


```
assign y = a & b;
```

- Use `always @ (*)` and blocking assignments (`=`) to model more complicated combinational logic if, case, for, etc. statements are useful
- Do not make assignments to the same signal in more than one `always` statement or continuous assignment statement.
  - Equivalent to driving one wire with multiple outputs
  - Assignment to Z is the only exception

 
# Blocking vs. Nonblocking Assignments

- `<=` is a “nonblocking assignment”
  - Occurs simultaneously with others
- `=` is a “blocking assignment”
  - Occurs in the order it appears in the file

```
// Good synchronizer using
// nonblocking assignments
module syncgood
  (input    clk,
   input    d,
   output reg q);
  reg n1;
  always @(posedge clk)
  begin
    n1 <= d; // nonblocking
    q  <= n1; // nonblocking
  end
endmodule
```


 
```
// Bad synchronizer using
// blocking assignments
module syncbad
  (input    clk,
   input    d,
   output reg q);
  reg n1;
  always @(posedge clk)
  begin
    n1 = d; // blocking
    q  = n1; // blocking
  end
endmodule
```



# Blocking and Non-Blocking Assignments

- Blocking assignments ( $Q = A$ )
  - variable is assigned immediately before continuing to next statement
  - new variable value is used by subsequent statements
- Non-blocking assignments ( $Q <= A$ )
  - variable is assigned only after all statements already scheduled are executed
    - value to be assigned is computed here but saved for later
  - usual use: register assignment
    - registers simultaneously take their new values after the clock tick
- Example: swap

```
always @(posedge CLK)
begin
    temp = B;
    B = A;
    A = temp;
end
```

```
always @(posedge CLK)
begin
    A <= B;
    B <= A;
end
```



ELSEVIER

# Swap (continued)

- The real problem is parallel blocks
  - one of the blocks is executed first
  - previous value of variable is lost

```
always @(posedge CLK)
begin
    A = B;
end
```

```
always @(posedge CLK)
begin
    B = A;
end
```

- Use delayed assignment to fix this
  - both blocks are scheduled by posedge CLK

```
always @(posedge CLK)
begin
    A <= B;
end
```

```
always @(posedge CLK)
begin
    B <= A;
end
```



# Non-Blocking Assignment

- Non-blocking assignment is also known as an RTL assignment
  - if used in an always block triggered by a clock edge
  - mimic register-transfer-level semantics – all flip-flops change together
- My rule: ALWAYS use <= in sequential (posedge clk) blocks

```
// this implements 3 parallel flip-flops
always @(posedge clk)
begin
    B = A;
    C = B;
    D = C;
end
```


```
// this implements a shift register
always @(posedge clk)
begin
    {D, C, B} = {C, B, A};
end
```

```
// this implements a shift register
always @(posedge clk)
begin
    B <= A;
    C <= B;
    D <= C;
end
```



# Finite State Machines

- Recall FSM model

 

- Recommended FSM implementation style
  - Implement combinational logic using a one always block
  - Implement an explicit state register using a second always block






# Verilog FSM - Reduce 1s example

- Change the first 1 to 0 in each string of 1's
  - Example Moore machine implementation

```
module reduce
  (input clk, reset, in,
   output reg out);

  // State assignment
  localparam ZERO = 0, ONE1 = 1, TWO1s = 2;
  reg [1:0] state, next_state;    // state register

   // Implement the state register
  always @(posedge clk)
    if (reset) state <= ZERO;
    else      state <= next_state;
```



# Moore Verilog FSM (cont'd)

```
always @(*) begin
  out = 0;      // defaults
  next_state = state;
  case (state)
    ZERO: begin          // last input was a zero
      if (in) next_state = ONE1;
    end

    ONE1: begin          // we've seen one 1
      if (in) next_state = TWO1S;
      else next_state = ZERO;
    end

    TWO1S: begin        // we've seen at least 2 ones
      out = 1;
      if (~in) next_state = ZERO;
    end
    // Don't need case default because of default assignments
  endcase
end
endmodule
```




# Mealy Verilog FSM for Reduce-1s example

```
module reduce
  (input clk, reset, in,
   output reg out);

  // State register
  localparam ZERO = 0, ONE = 1;
  reg state, next_state; // state register
  always @(posedge clk)
    if (reset) state <= ZERO;
    else      state <= next_state;

   always @(*)
    out = 0;
    next_state = state;
    case (state)
      ZERO: // last input was a zero
        if (in) next_state = ONE;
      ONE: // we've seen one 1
        if (in) begin
          out = 1;
        end else begin
          out = 0;
          next_state = ZERO;
        end
    endcase
endmodule
```



# Restricted FSM Implementation Style

- Mealy machine requires two always blocks
  - register needs posedge CLK block
  - input to output needs combinational block
- Moore machine can be done with one always block
  - e.g. simple counter
  - Not a good idea for general FSMs
    - Can be very confusing (see example)
- Moore outputs
  - Share with state register, use suitable state encoding