

CSEP567: Design and Implementation of Digital Systems– Focus on Embedded Design

- Course staff:
 - Bruce Hemingway and Waylon Brunette, with Chris Grand
- Course web:
 - <http://www.cs.washington.edu/education/courses/csep567/05au/>
 - My office: CSE 464 Allen Center, 206 543-6274
- Today
 - Grading
 - Technology Timeline
 - Electrical basics
 - AVR I/O

CSEP567

Microcontrollers

1

Grading (our current thinking)


- Lab Completion: 50%
- Assignments: 30%
- Take-home exam/report/class participation: 20%

CSEP567

Microcontrollers

2


Technology timeline

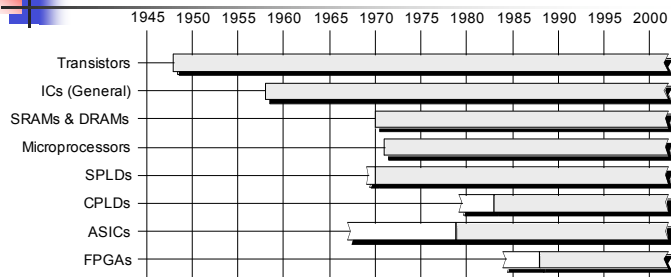

3

1854

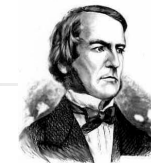- George Boole
 - Boolean algebra
 - Number system with 2 values
 - 0/1 \Leftrightarrow false/true
 - Do math on logic statements
 - 3 operations (NOT, AND, OR)



All computers use
Boolean algebra

NOT

A	Out
0	1
1	0

AND

A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1


OR


A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

4

1938

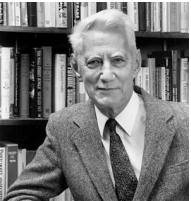
- Claude Shannon
 - Implemented Boolean algebra using switches
 - Described information using binary digits (bits)



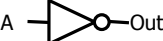


NOT

A	Out
0	1
1	0

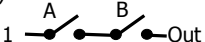

AND

A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

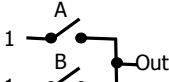


OR

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1


5

1937

- Alan Turing
 - Turing Machines
 - Simple computer model
 - Can something be computed?




Also pioneered artificial intelligence

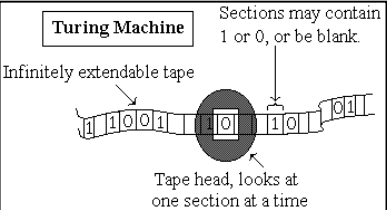

6

1945

- John von Neumann
 - First stored computer program
 - A sequence of operations
 - Read from memory
 - Operate using logic gates
 - Store result into memory





Other contributions:
Quantum Mechanics
Cellular Automata
Game Theory

7

1965

- Gordon Moore
 - Moore's Law: The transistor density of silicon chips doubles every 18 months

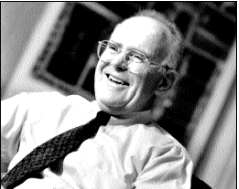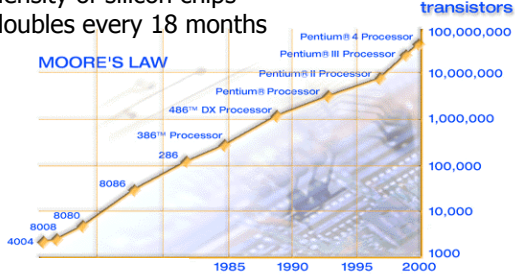
8

1971




Ted Hoff invents the microprocessor

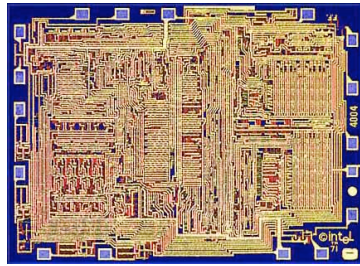- Intel 4004
- 2,300 transistors
- 3 mm by 4 mm
- As powerful as the ENIAC




9

Hardware + Software + Technology

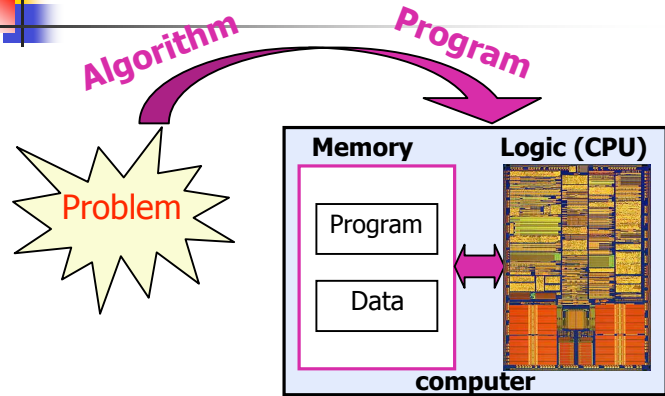


10

Technology timeline




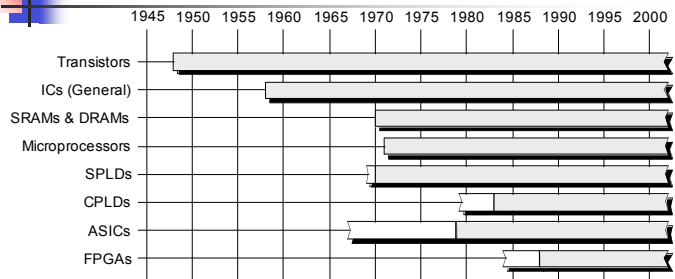





11

Programmable Logic Devices

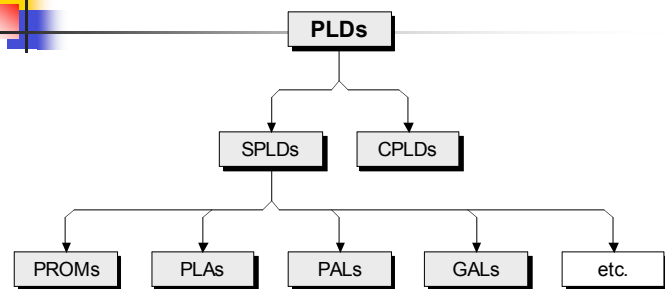

12

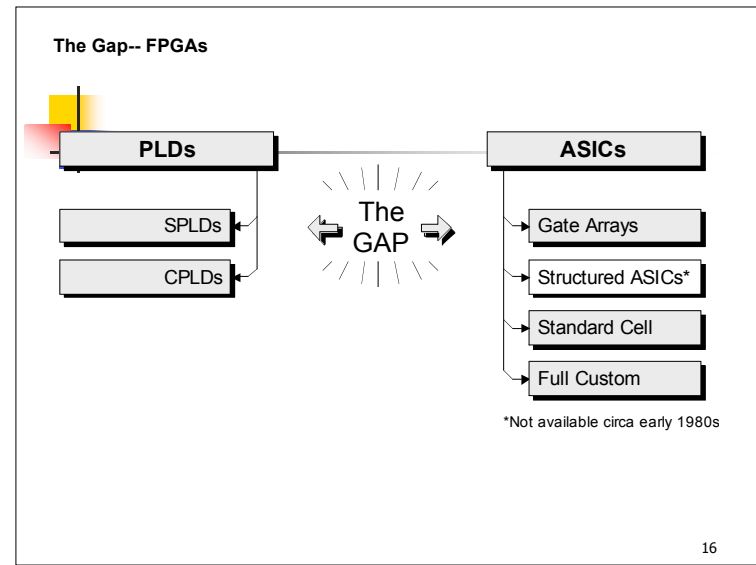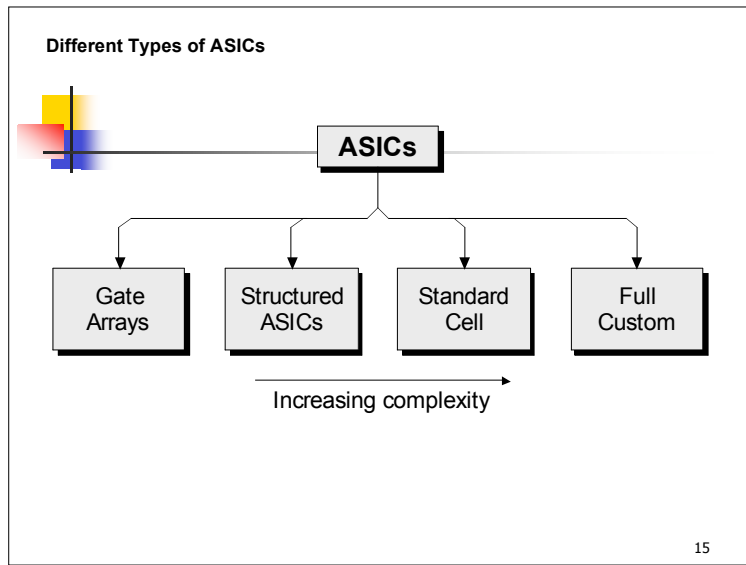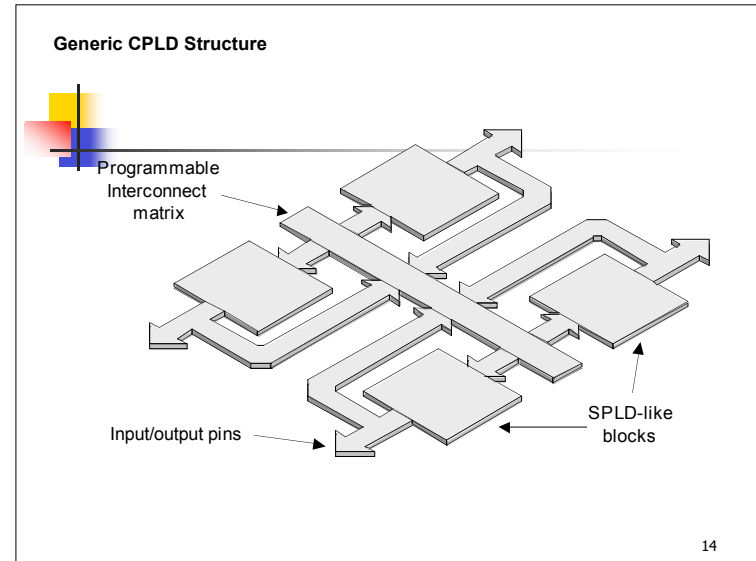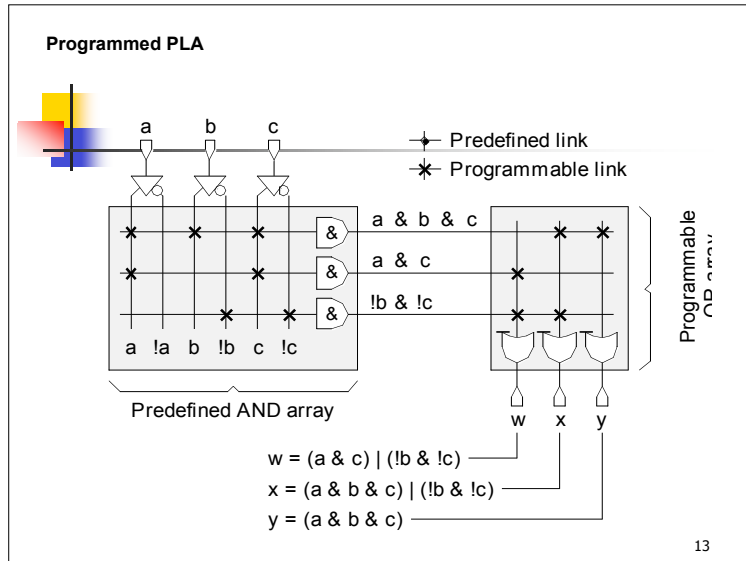

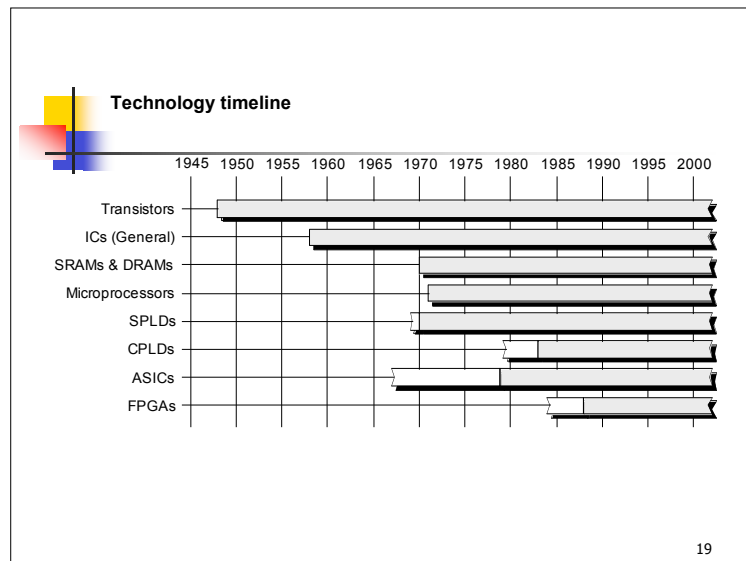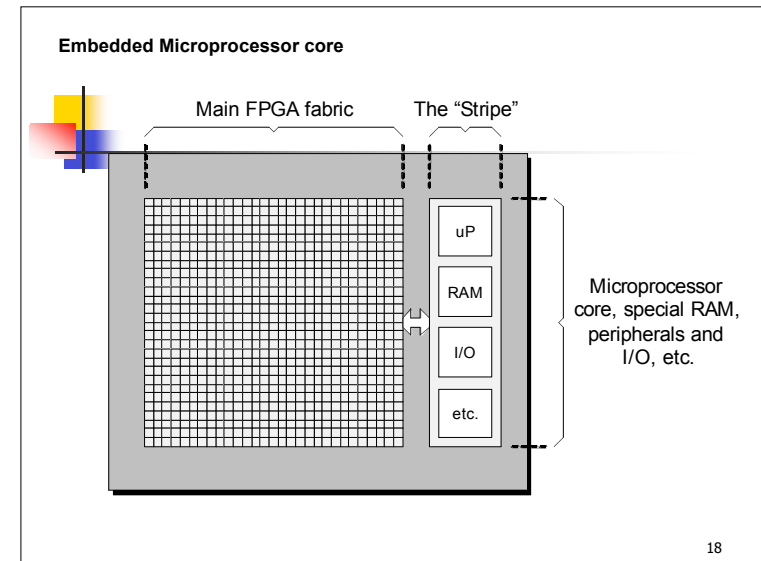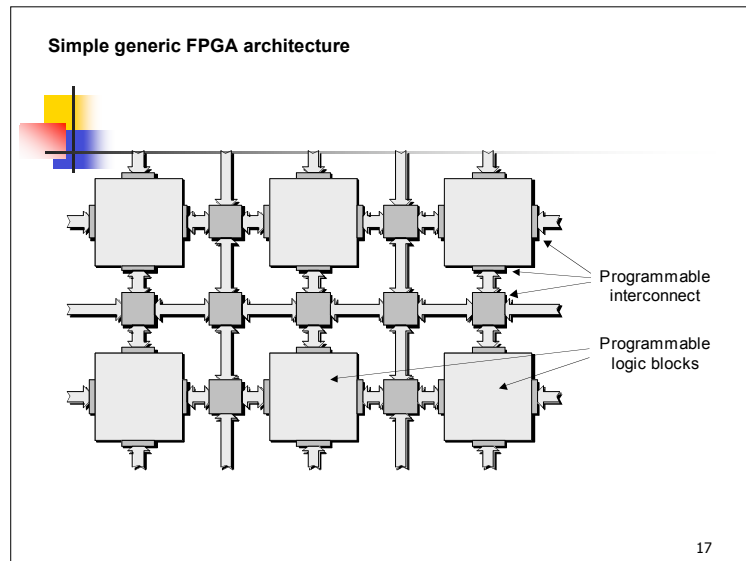

Charge

Two hydrogen atoms meet. One says "I've lost my electron."


The other says "Are you sure?"

The first replies "Yes, I'm positive."

20

Basic Concepts of Electricity

- Voltage
- Current
- Resistance

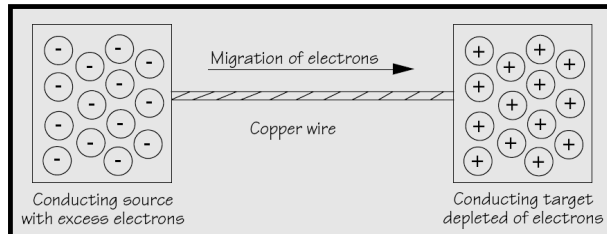

21


Electric Fields

- An electric field applies a force to a charge
 - Force on positive charge is in direction of electric field, negative is opposite
- Charges move if they are mobile
- An electric field is produced by charges (positive and negative charges)
- Electric fields can be produced by time varying magnetic fields (generator, antenna radiation)

22

Voltage Difference

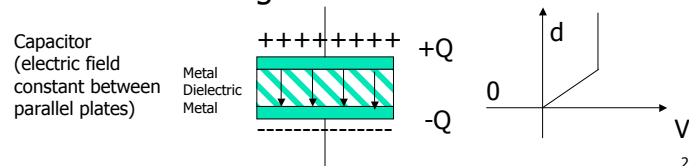- Voltage difference is the difference in potential energy in an electric field
- $E = V/d$
- As you move closer to a positive charge the voltage increases



23

Current

- An electric current is produced by the flow of electric charges
- Current = rate of charge movement
= amount of charge crossing a surface per unit time
- In conductors, current flow is due to electrons
- Conventional current is defined by the direction positive charges will flow
- Direction of electron flow is opposite to direction of conventional current


24

Resistance

- In materials electrons accelerate in an electric field
- Electrons lose energy when they hit atoms - lost energy appears as heat and light
- The result is that electrons drift with constant velocity (superimposed on random thermal motion)
- Resistance is the ratio Voltage/current
 $R = V/I$

25

Voltage, Current, and Resistance

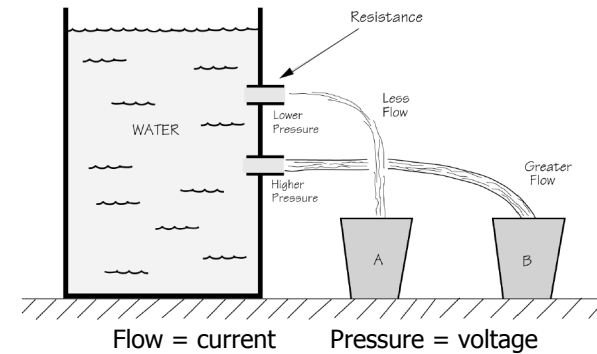


26

Material Conductivity

- Conductors - negligible resistance
- Insulators - extremely large resistance
- Semiconductors - some resistance
- Resistors - are devices designed to have constant resistance across a range of voltages


27

Resistor Combination

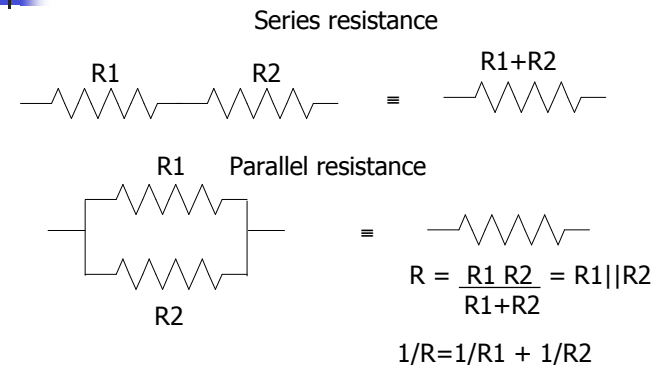

28


Voltage Divider

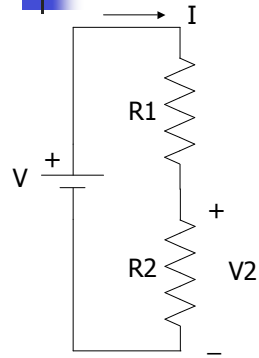

$$V_2 = \frac{V R_2}{R_1 + R_2}$$

29

Potentiometer (Variable Resistor)

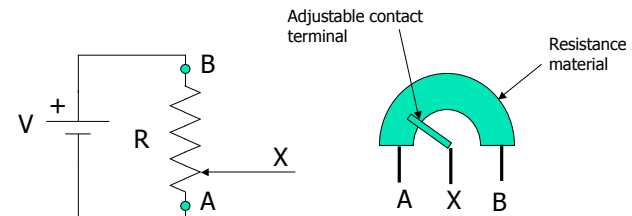

$$V_X = V * \text{Distance AX} / \text{Distance AB}$$

(linear potentiometer)

A trimpot is a small variable resistor mounted on a printed circuit board that can be adjusted by a small screwdriver to make semi-permanent adjustments to a circuit


30

Capacitors

- A component constructed from two conductors separated by an insulating material (dielectric) that stores electric charge (+Q, -Q)
- As a consequence there is a voltage difference across the capacitor, V
- Capacitance = $C = Q/V$
- The dielectric material operates to reduce the electric field between the conductors and so allow more charge to be stored for a given voltage

31


Capacitors

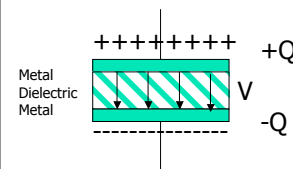

$$C = Q/V$$

$$(Q = CV)$$


Bucket analogy

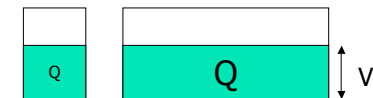

A small bucket (capacitor, C) holds less charge (Q) for given level (voltage V) than a large bucket

32

Charging a Capacitor

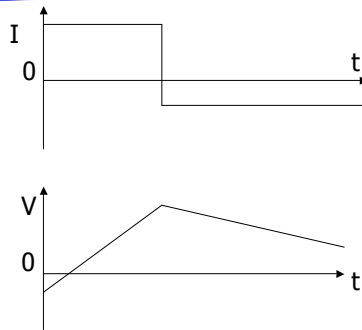


The bucket analogy can be used to describe capacitor charging

When current flows in at a constant rate the voltage increases linearly and vice versa for current flowing out

33

Semiconductors

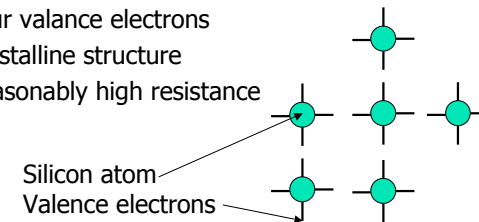- Silicon is used as an example (other semiconductors include Germanium, Gallium Arsenide, Gallium phosphide, indium arsenide, indium phosphide)
- Pure silicon (intrinsic semiconductor)
 - Four valence electrons
 - Crystalline structure
 - Reasonably high resistance



34


Electrons and holes

- Due to thermal energy some electrons in the valance shell become free
- Create:
 - One free electron +
 - One hole in the valance band that can be filled by electrons from the valance band in an adjacent silicon atom
- Current in silicon can flow due to both movement of electrons and holes

35

n-type silicon

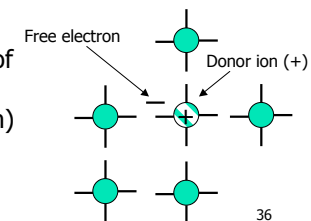
- Add donor impurities (e.g. Phosphorus, arsenic, indium) with 5 electrons in the valance band
- As only four electrons can bond with neighbouring silicon atoms one free electron is left
- Increases concentration of free electrons
- Reduces concentration of holes (due to increased chance of recombination)
- Resistance reduced



36

p-type silicon

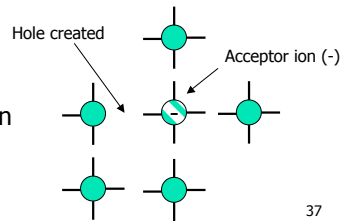
- p-type silicon is created by adding acceptor impurities which have three valence electrons (e.g. boron)
- This leaves an unbound valence electron in an adjacent silicon atom creating a hole
- Increases concentration of holes
- Reduces concentration of free electrons
- P-type silicon has lower resistance than pure silicon



37

Diodes

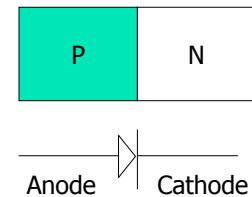- If a piece of n-type silicon and p-type silicon are joined directly together a diode (di - electrode) device is created



38


Macro-behaviour

- A diode is a device that allows current flow easily in one direction easily and allows hardly any current flow in the opposite direction

39

Forward bias

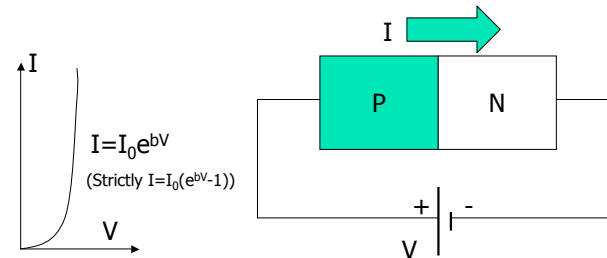
- Current flows easily if the P region is positive with respect to the N region



40


Reverse bias

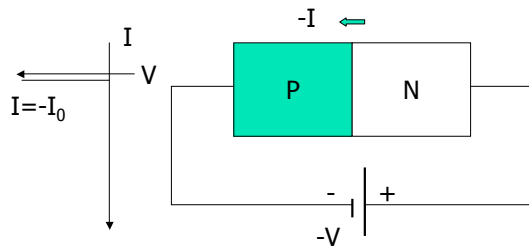- Current hardly flows if the P region is negative with respect to the N region



41

Diode and resistor circuit

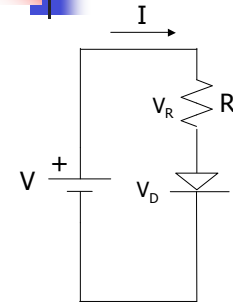

Currents and voltages determined by:
(work backwards to find V_D)

- V_D related to I by diode equation
- Current in resistor and diode equal
- $V_R = IR$
- voltage across diode and voltage resistor add up to voltage source V


Short cut rule of thumb, V_D is approx 0.6-0.7 volts and $V_R \approx V - 0.6$

For LEDs V_D is about 1.8 - 4.0 V, depending on color

Forward biased diode

42

Diode and resistor circuit

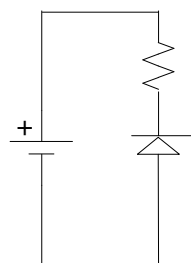

Assume no reverse-bias current flows (ideal case)

Therefore no voltage occurs across the resistor

Therefore the full supply voltage appears across the diode

Reverse biased diode

43

LEDs

- Light emitting diode
- When an electron moves down from the conduction band to the valence band it loses energy
- In silicon and germanium the energy-momentum relationships mean that this energy is lost heat
- In gallium arsenide it produces a photon

44

LEDs

- The light intensity is proportional to current
- Pure gallium arsenide produces infrared light
- GaAsP produces red or yellow light
- GaP produces red or green


45

Circuit design using LEDs

- LEDs behave just like normal diodes except that the forward bias voltages are greater (typically 1.8 - 4.0 V)
- A typical forward bias current of 10-20 mA is used.

46

Example

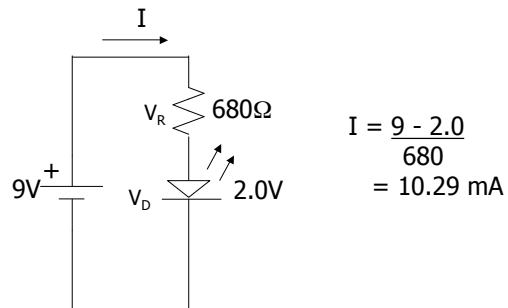


47

AVR I/O

Atmel AVR Microcontroller

48

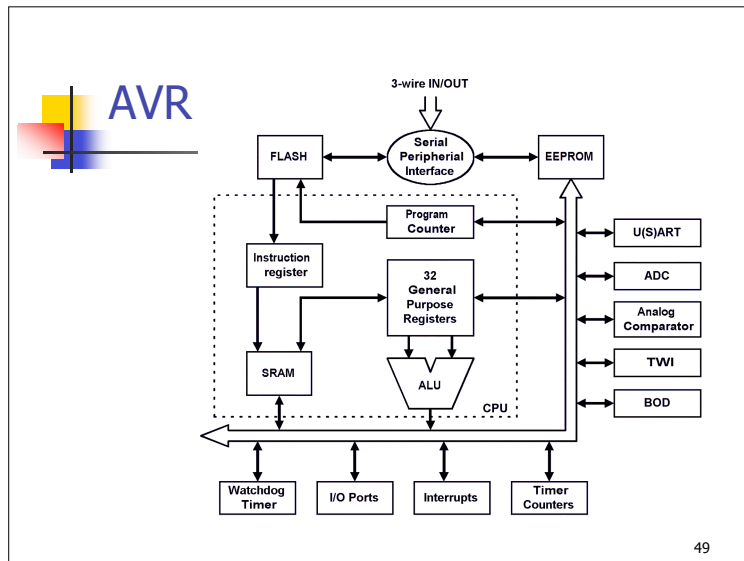

49

ATmega16(L)

- 40/44 pin packages
- 16 KBytes ISP Flash, Self Programmable
- 512 Bytes ISP EEPROM
- 1 KBytes SRAM
- Full Duplex UART
- SPI – Serial Interface
- TWI – Serial Interface
- 8- and 16-bits Timer/Counters with PWM
- 2 External Interrupts
- 10-bit ADC with 8 Multiplexed Inputs
- RTC with Separate 32 kHz Oscillator
- Analog Comparator
- JTAG Interface with On-Chip Debugger

50

I/O Ports General Features





- Push-Pull Drivers
- High Current Drive (sinks up to 40 mA)
- Pin-wise Controlled Pull-Up Resistors
- Pin-wise Controlled Data Direction
- Fully Synchronized Inputs
- Three Control/Status Bits per Bit/Pin
- Real Read-Modify-Write

51

3 Control/Status Bits per Pin

- DDx Data Direction Control Bit
- PORTx Output Data or Pull-Up Control Bit
- PINx Pin Level Bit

52

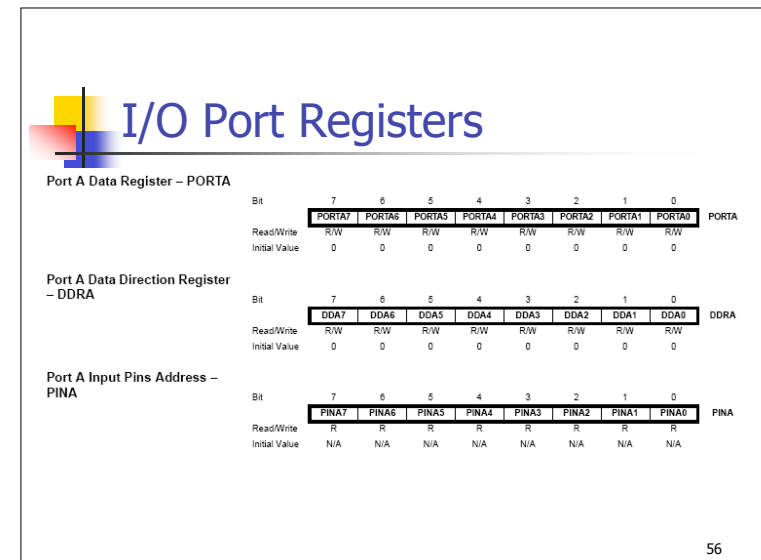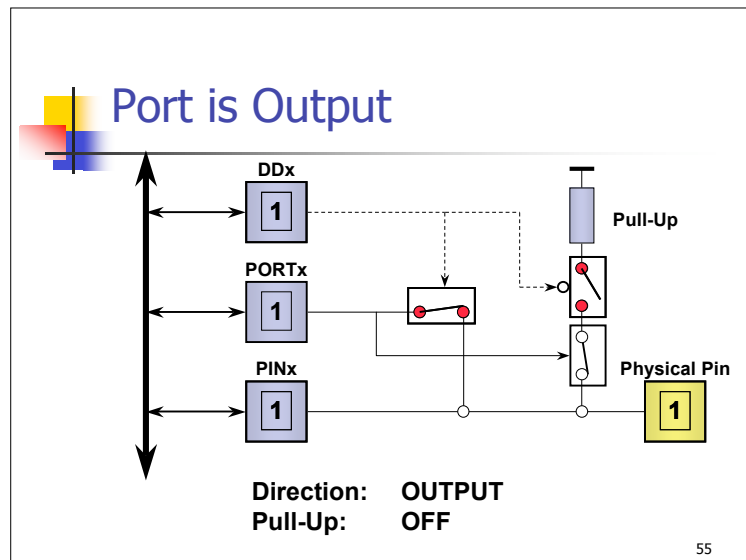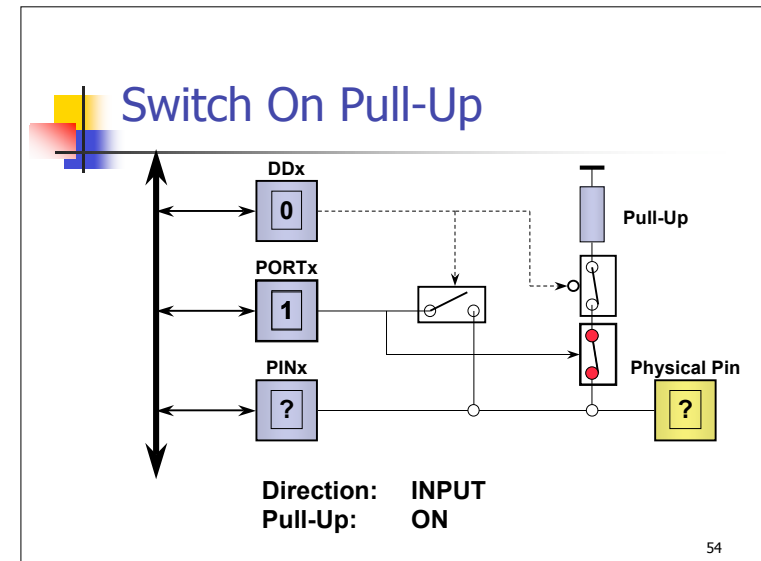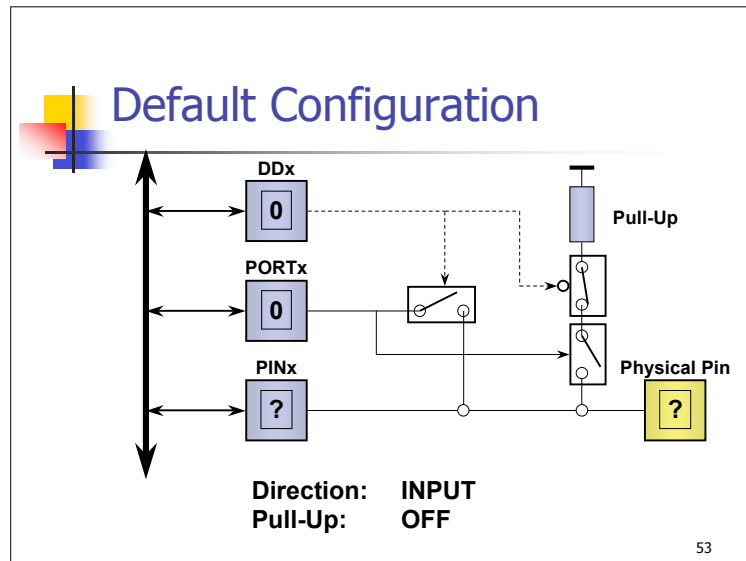

Sample Code from Lab 1

```

.include "C:\Program Files\Atmel\AVR
Tools\AvrAssembler\Appnotes\m16def.inc"

.cseg
ldi r16, 0xff
out DDRB, r16
ldi r16, 0x00
out PORTB, r16
loop:
jmp loop

```

